




Switched Capacitor Power Amplifiers: Powering the Next Generation of Wireless Communication, from RF to mm-Wave

Jeff Walling

Virginia Tech


- **Background and Motivation**
- Switched-Capacitor Power Amplifier (SCPA) Introduction
- Recent Demonstrations of SCPAs
- mmWave SCPAs
 - Frequency multiplying class-D
 - Frequency multiplying SCPA
- Conclusions

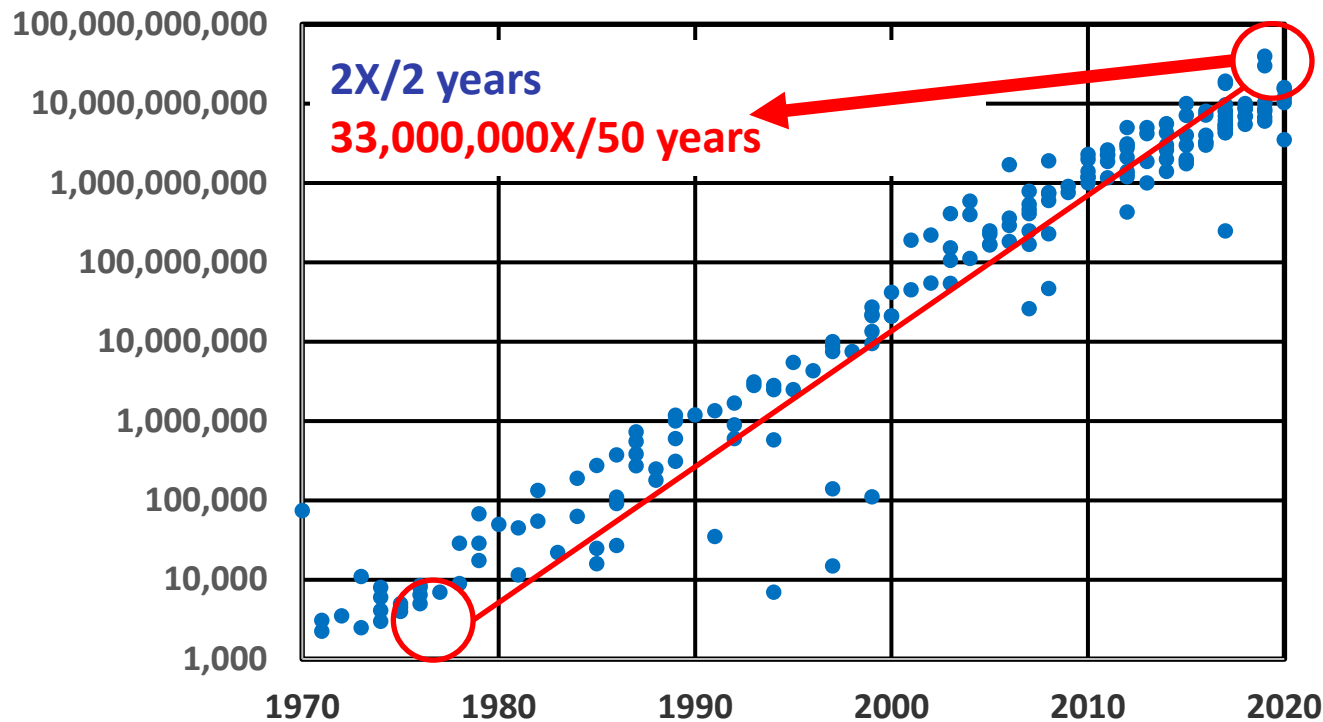Data source: https://en.wikipedia.org/wiki/Transistor_count
Microprocessor Transistor Counts



- Scaling CMOS
 - Faster, lower loss switch
 - Reduced intrinsic gain
- Architectural Changes in Analog/RF/Mixed-Signal Circuits
 - More Digital Circuits
 - Fewer Analog Blocks (e.g., Amplifiers)

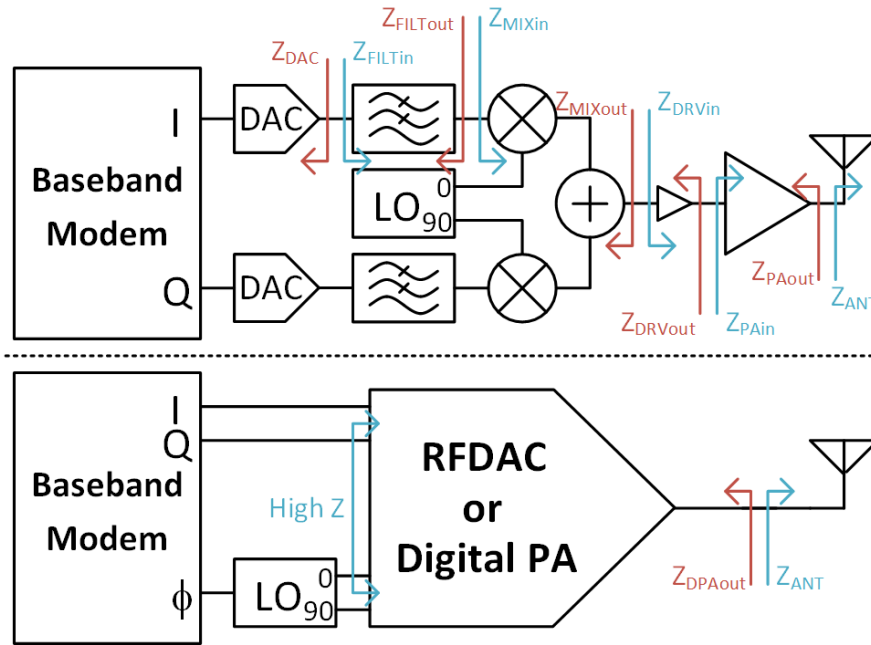
Goal: Use transistors as switches, or find architectures that do well with reduced precision




Analog Interfaces at DAC, Filter, Mixer, Driver, PA, Antenna

Switching Interfaces everywhere but DPA-to-Antenna

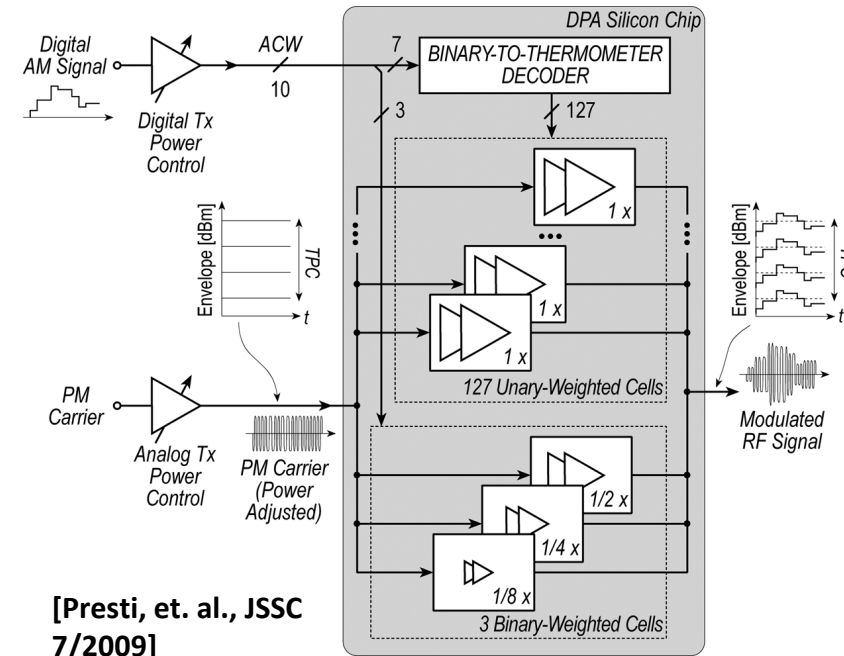
- Conventional TX: impedance, linearity, noise, gain specs at every interface; driven by analog performance
- Digital PA: high-impedance gate interfaces; driven by digital switching performance



IDPA = Current DPA

 


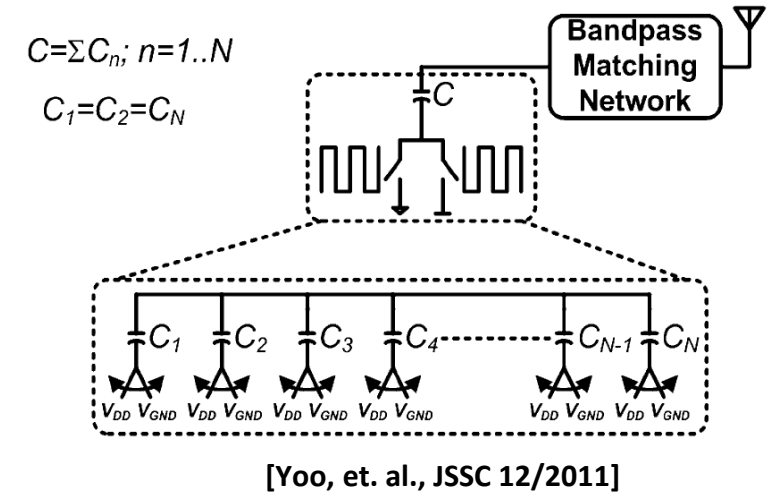VDPA = Voltage DPA
SCPA = Switched-capacitor PA



- Sometimes called “RF-DAC”, “DPA=Digital PA”
 - A DAC (Converts complex digital-signal to RF-signal)
 - A Mixer (Translates signal from baseband to RF)
 - An Output Stage (PA Predriver or PA)

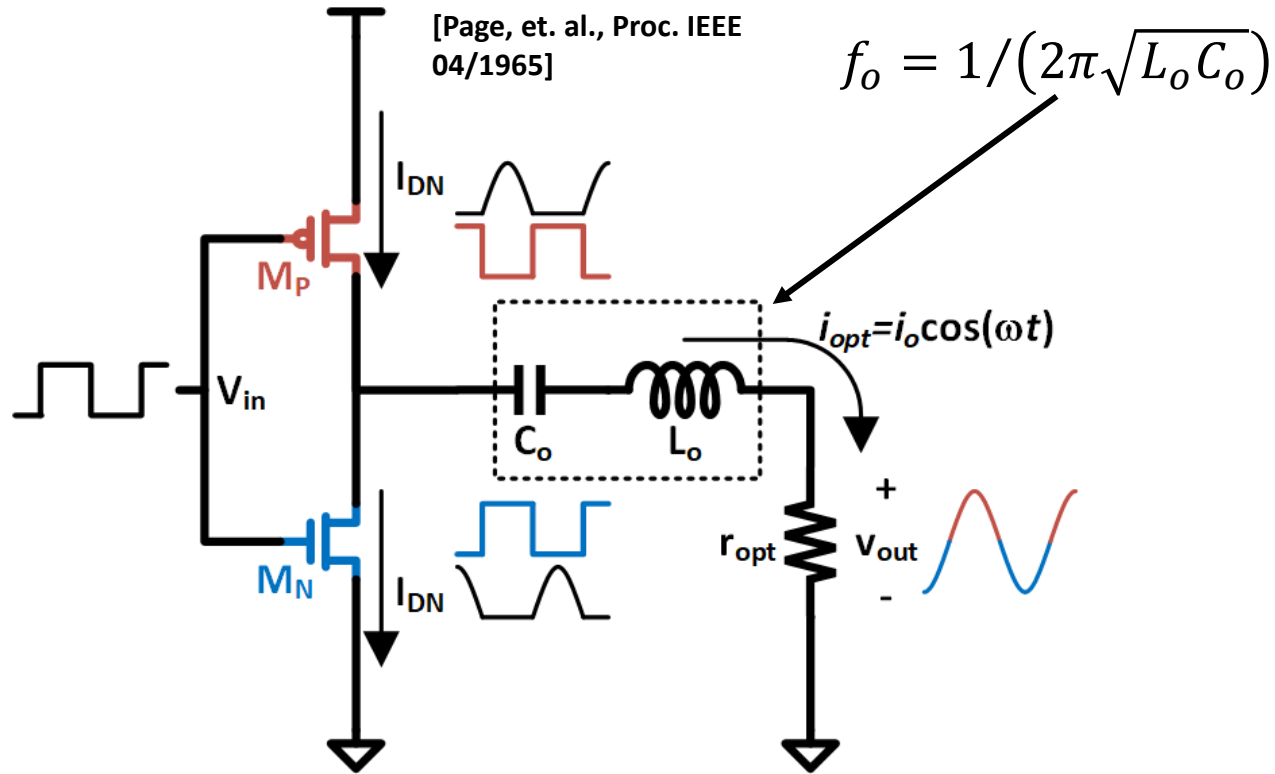- Background and Motivation
- **Switched-Capacitor Power Amplifier (SCPA) Introduction**
- Recent Demonstrations of SCPAs
- mmWave SCPAs
 - Frequency multiplying class-D
 - Frequency multiplying SCPA
- Conclusions



□ Output Power:

$$P_{out} = \frac{2}{\pi^2} \frac{V_{DD}^2}{r_{opt}}$$

□ Drain Efficiency:


$$\eta = 100\%$$

□ R_{opt} :

$$r_{opt} = \frac{2}{\pi^2} \frac{V_{DD}^2}{P_{out}}$$

- CMOS Inverter + Series Resonant Filter
- Input is driven with CE pulse train
- Reduces Drain Voltage/Current Overlap $\rightarrow \eta=100\%$

[Page, et. al., Proc. IEEE
04/1965]

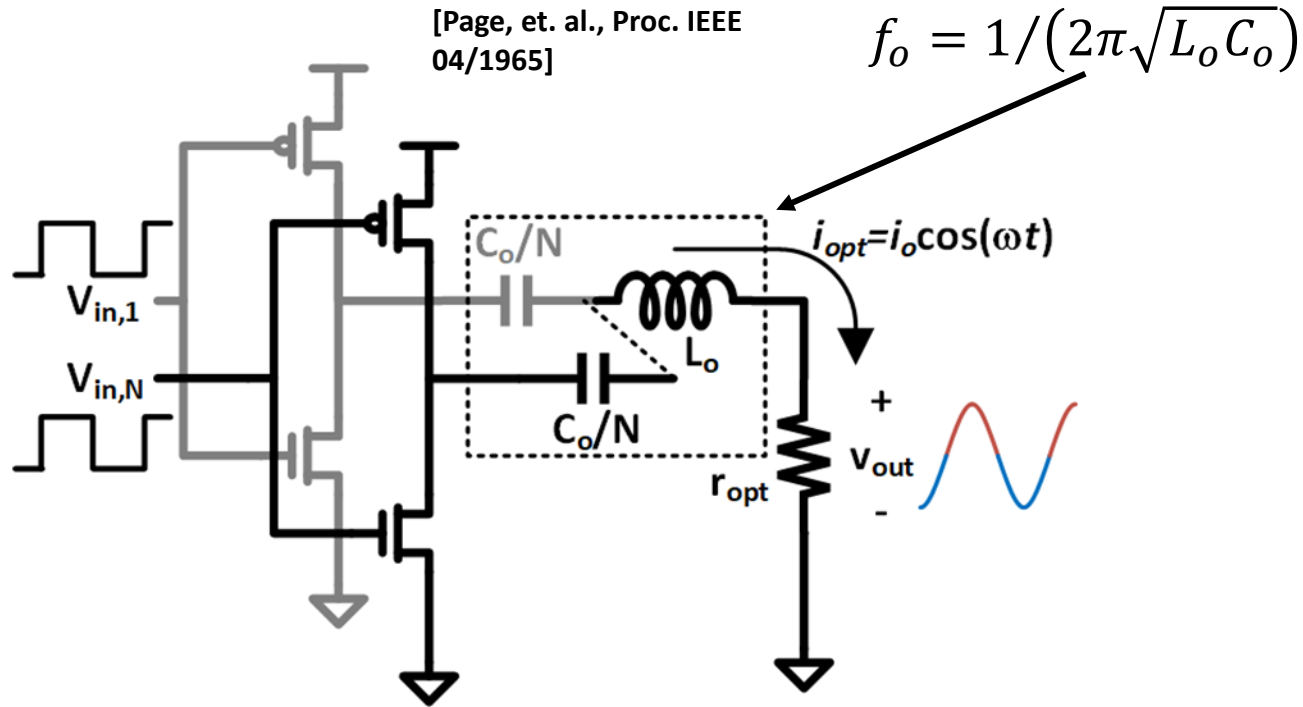

□ Output Power:

$$P_{out} = \frac{2}{\pi^2} \frac{V_{DD}^2}{r_{opt}}$$



□ Drain Efficiency:

$$\eta = 100\%$$

□ R_{opt} :

$$r_{opt} = \frac{2}{\pi^2} \frac{V_{DD}^2}{P_{out}}$$

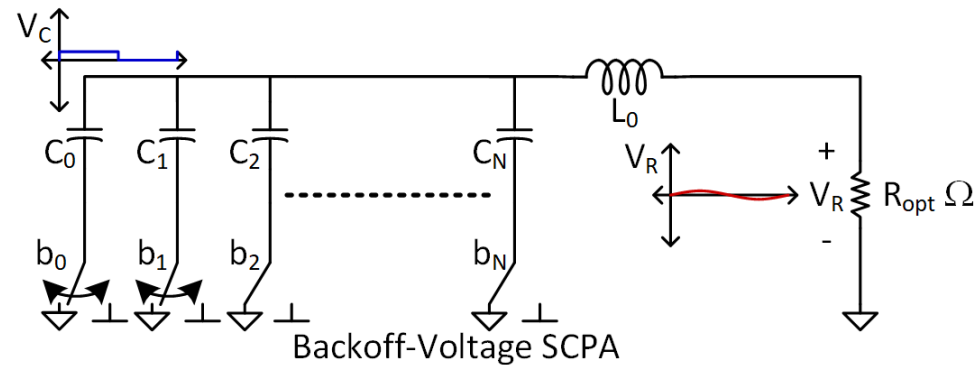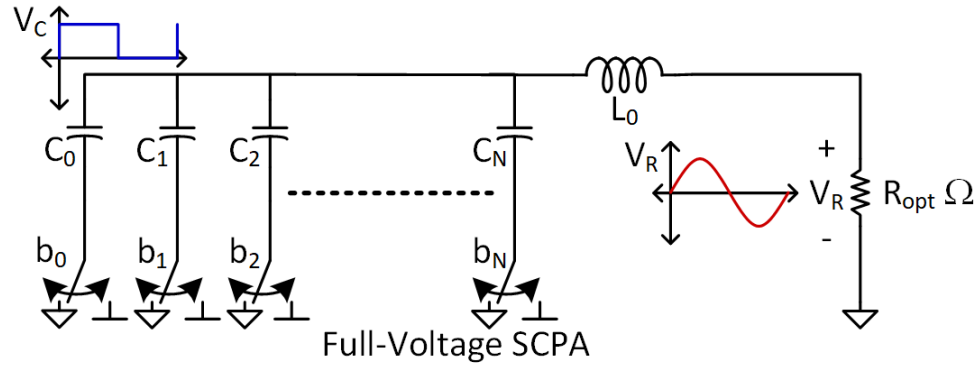- In CMOS switches and capacitors can be sub-divided
 - Slices can be unary ($\div N$) or binary ($\div 2^N$) weighted
- When all slices are switched, circuit is equivalent to class-D PA
- Resonance constant if RC product from switch-capacitor constant



Unit Capacitance:

$$C_N = C_U = \frac{C}{N}$$

[Yoo, et. al., JSSC 12/2011]

Switch at V_{DD} :

$$Q_1 = nC_U V_{DD}$$

Switch at V_{GND} :



$$Q_2 = NC_U V_C$$

Charge Conservation:


$$Q_1 = Q_2$$

$$V_C = \frac{n}{N} V_{DD}$$

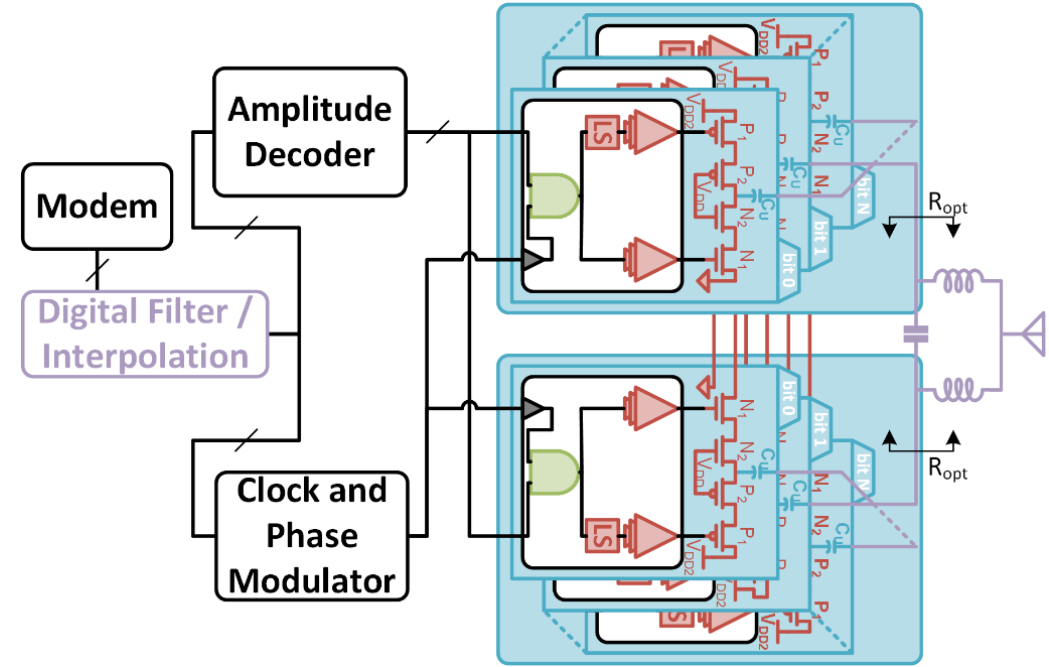 - Voltage at capacitor top-plate changes due to charge-redistribution
- Very linear \rightarrow precision capacitors and switches in CMOS
- Can model switch as variable-voltage switch!



 
- DAC + Filter + Mixer + Amplifier + RF Filter
- All blocks Mixed-Signal/Analog/RF
- Filter is at Analog Baseband
- Digital Filter + Mixer + Amplifier + DAC + RF Filter
- All SCPA blocks realized by switching
- Filter at RF and Digital Baseband



[Walling, et. al., RFIC-VJ 12/2018]

- Thevenin Eq.: variable voltage switch in series with RLC
- RLC tuned to switch closure frequency, f_{RF}
 - Selects fundamental Fourier component of pulsed V:
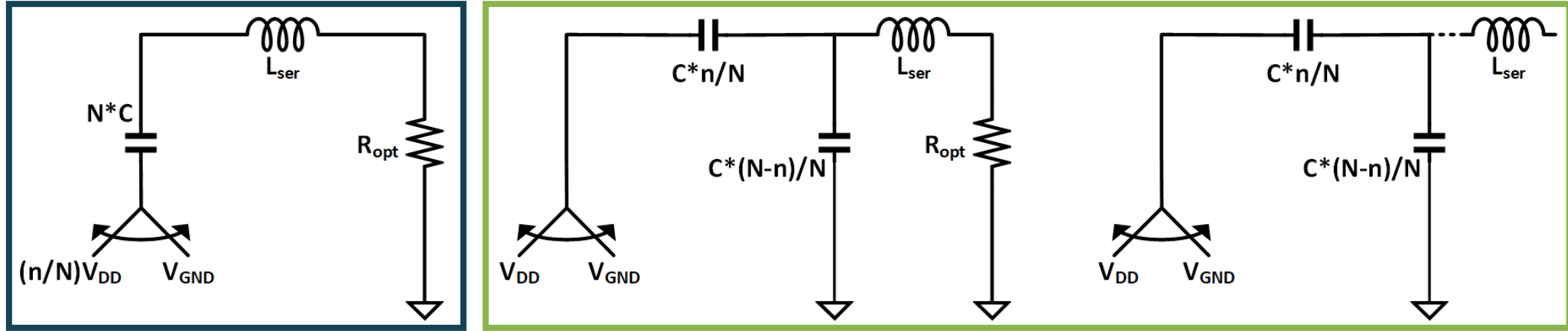
$$V_{out} = \frac{1}{2} \frac{4}{\pi} \left(\frac{n}{N} \right) V_{DD} \quad P_{out} = \frac{2}{\pi^2} \left(\frac{n}{N} \right)^2 \frac{V_{DD}^2}{R_{opt}}$$



[Walling, et. al., RFIC-VJ 12/2018]

- Input power: $\propto C_{in} V_{DD}^2 f_{RF}$
- L_{ser} is RF current source \rightarrow Open if switch closure is fast
- Input capacitance: $C_{in} = C \frac{N-n}{N^2}$


$$V_{out} = \frac{1}{2} \frac{4}{\pi} \left(\frac{n}{N}\right) V_{DD} \quad P_{out} = \frac{2}{\pi^2} \left(\frac{n}{N}\right)^2 \frac{V_{DD}^2}{R_{opt}}$$

$$P_{in} = C \left(\frac{n - N}{N^2}\right) V_{DD}^2 f_{RF}$$

• SCPA Total Power Consumption:

- Lossy inductor: α
- SW parasitic R: β
- SW parasitic C: $P_{SWC} = (n/N) C_{SW} V_{DD}^2 f_{rf}$
- Switch driver: $P_{DR} = (n/N) C_{DR} V_{DD}^2 f_{rf}$
- Clock distribution: $P_{CLK} = C_{CLK} V_{DD}^2 f_{rf}$
- Logic Decoders: $P_{Logic} = C_{Logic} V_{DD}^2 f_{rf}$

Benefit from scaling

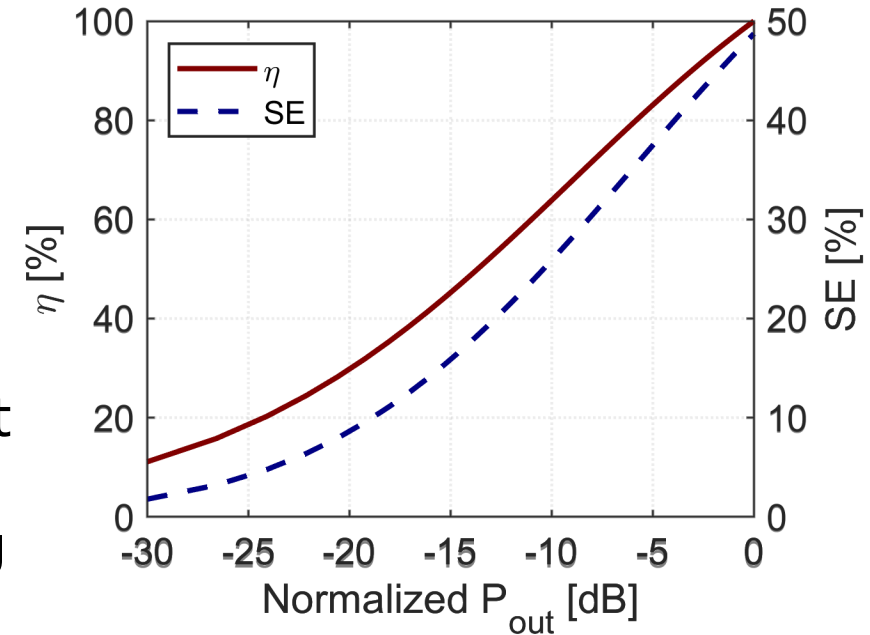


$$\eta = \frac{P_{out}}{P_{out} + P_{in}} = \frac{4n^2}{4n^2 + \frac{\pi n(N-n)}{Q_{NW}}}$$

$$Q_{NW} = \frac{1}{2\pi f_{RF} C r_{opt}} = \sqrt{\frac{50\Omega}{r_{opt}} - 1}$$


$$SE = \frac{\alpha \cdot \beta \cdot P_{out}}{P_{out} + P_{in} + P_{SWC} + P_{DRV} + P_{CLK} + P_{Logic}}$$
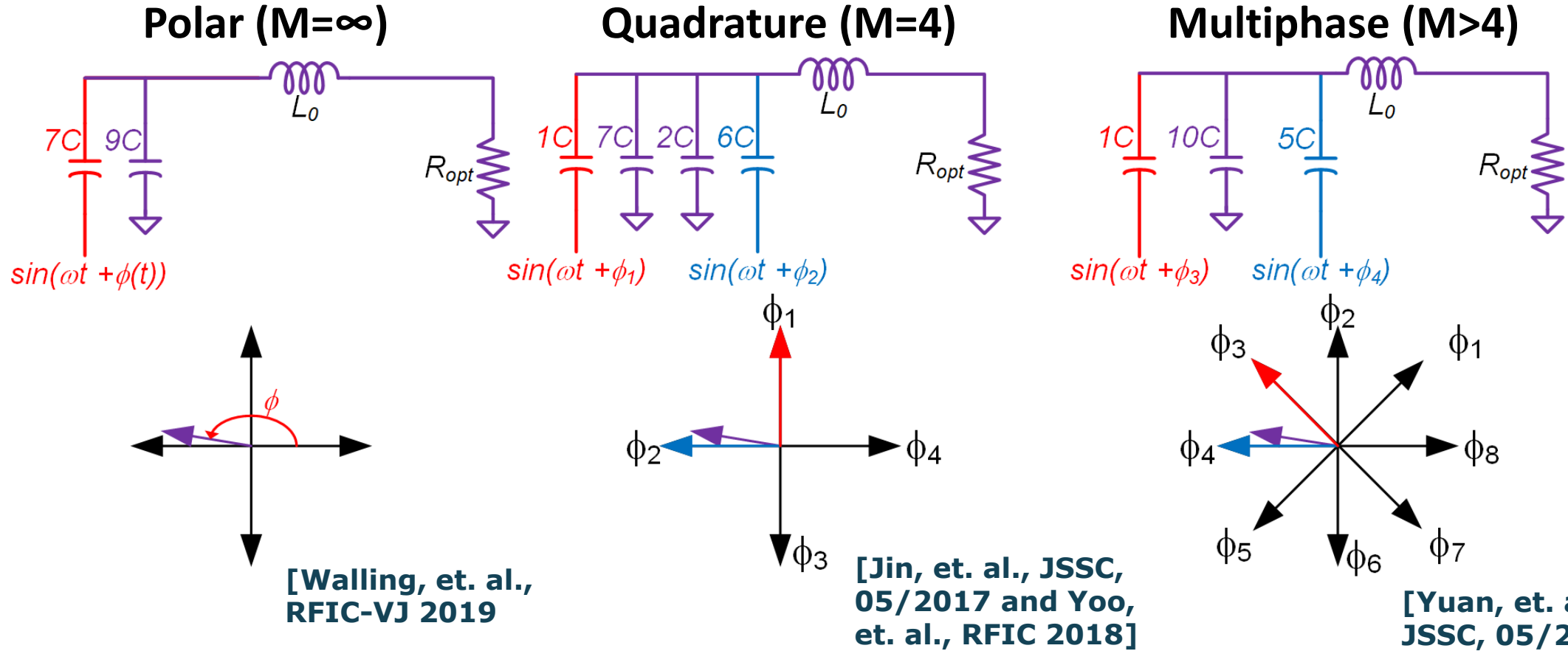
$$\alpha = \frac{1}{1 + \frac{Q_{nw}}{Q_L}} \quad \beta = \left(\frac{R_{opt}}{R_{sw} + R_{opt}} \right)^2$$




- Polar → Multi-phase: Rather than phase shift clock, switch capacitors on different phases with arbitrary weights



 
- Background and Motivation
- Switched-Capacitor Power Amplifier (SCPA) Introduction
- **Recent Demonstrations of SCPAs**
- mmWave SCPAs
 - Frequency multiplying class-D
 - Frequency multiplying SCPA
- Conclusions



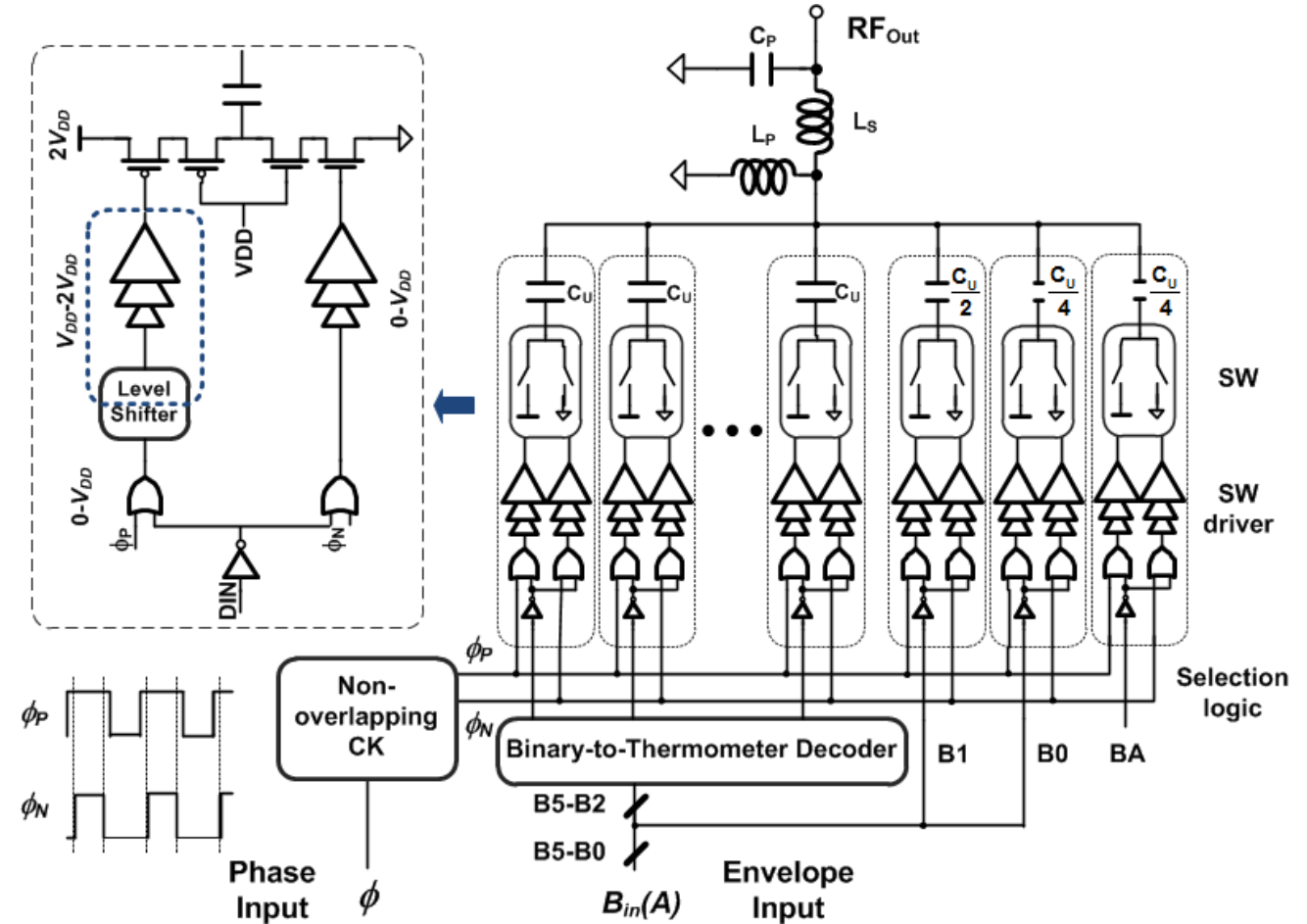
- First voltage-mode DPA!
- 90nm 6b segmented (4bU + 2bB) array
- Cap array in MiM layer
- Cascoded switch \rightarrow higher η




[Yoo, et. al., JSSC 12/2011]

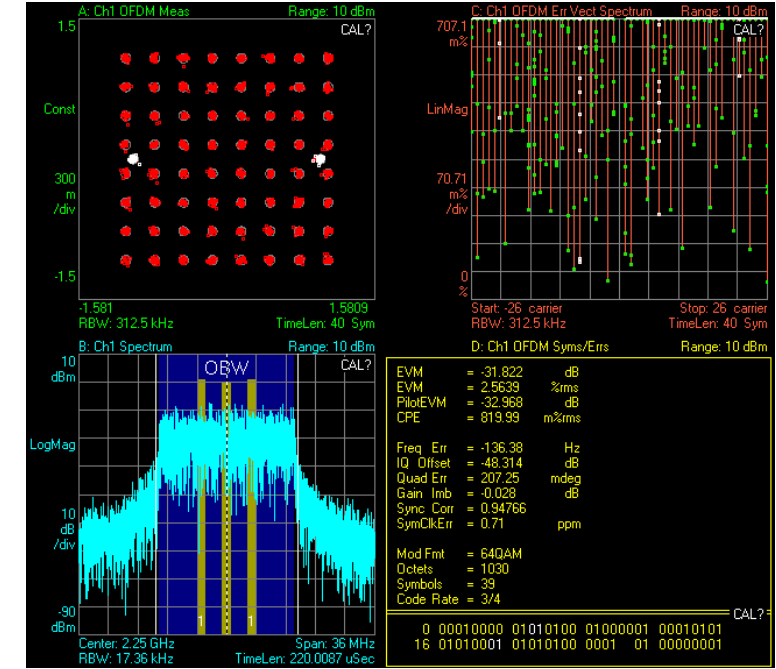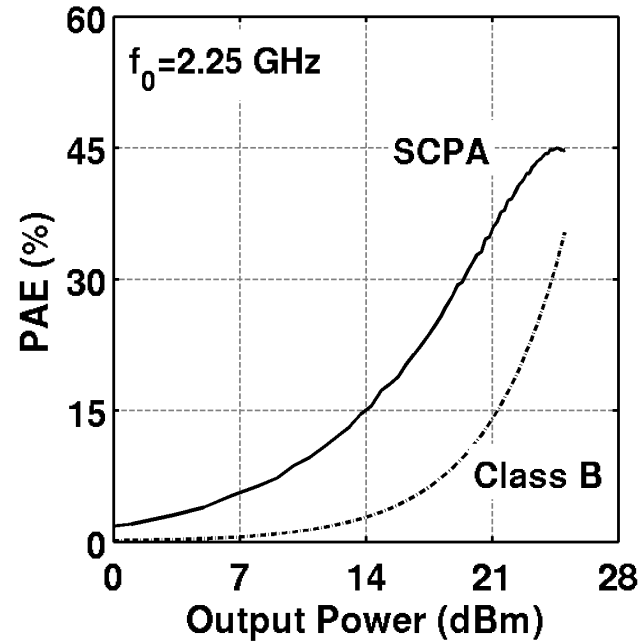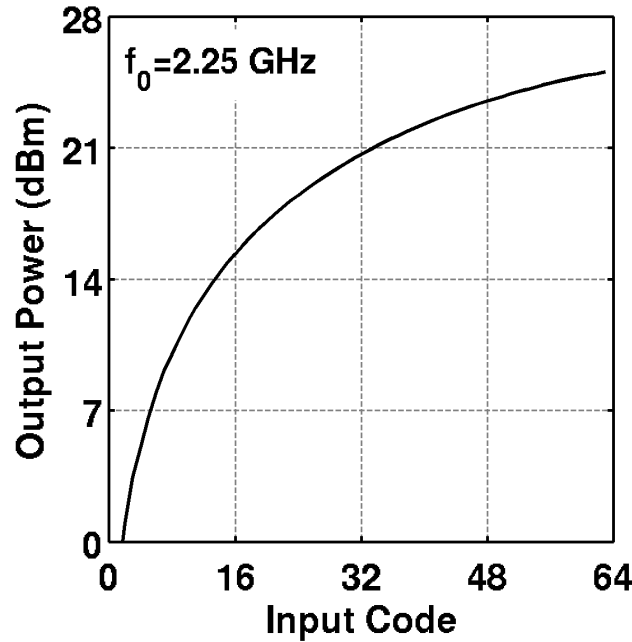

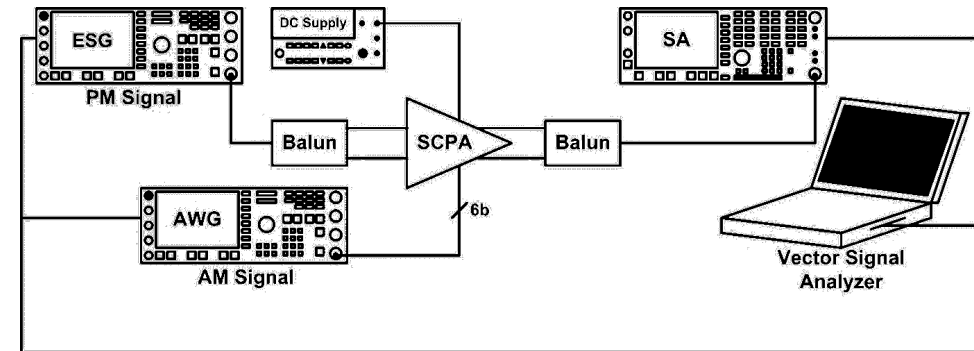- EVM = 2.6%-rms @ $P_{out} = 17.7 \text{ dBm}$ (SE = 27%)
- Phase Modulation input from ESG
- Amplitude Modulation → digital pattern generator




Example: Cartesian SCPA - I

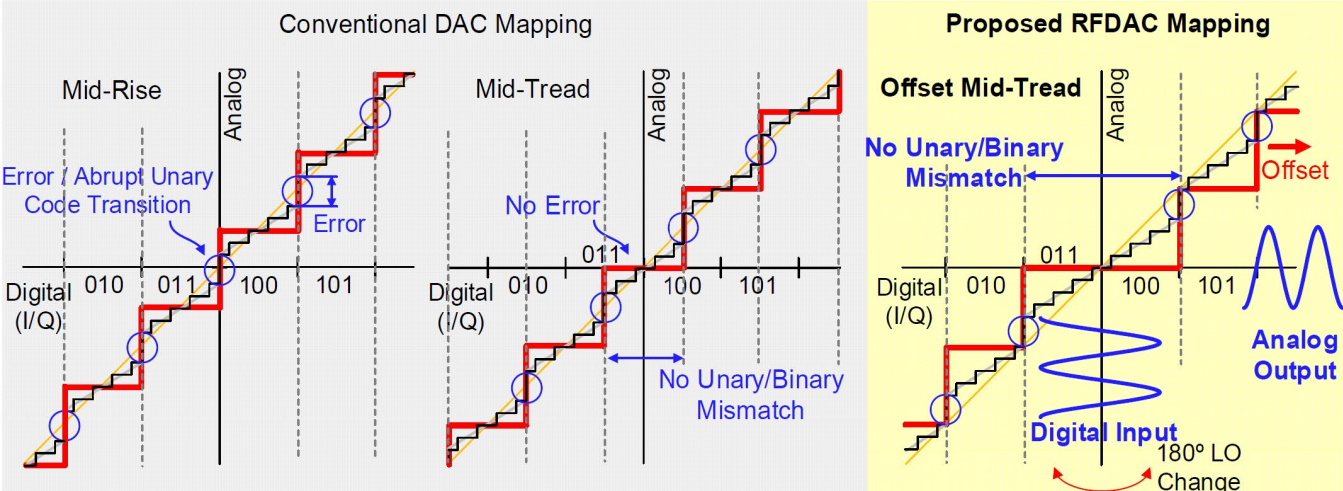

- Segmented DACs have large errors during unary → binary transitions
- Error is similar when using traditional DAC code mapping


[Yoo, et. al., ISSCC 2020]

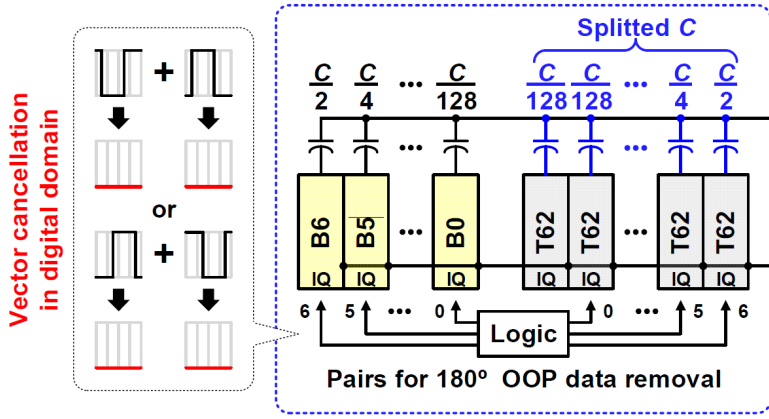
- Can modify the mapping by driving cells anti-phase so that their charge cancels!




Unary to binary cell splitting
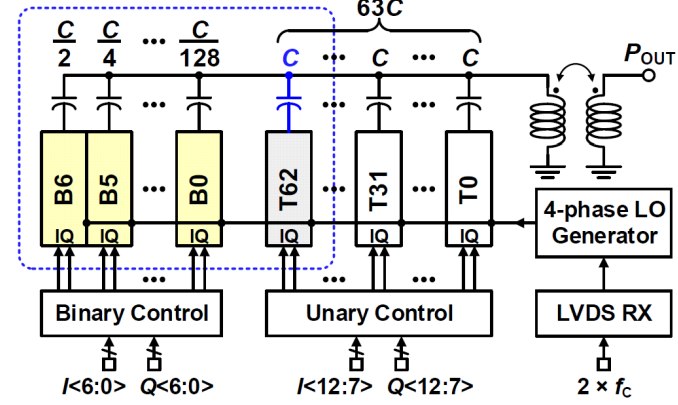
$$C = C \sum_{k=1}^7 (1/2)^k + \frac{C}{128}$$




 

[Yoo, et. al., ISSCC 2020]

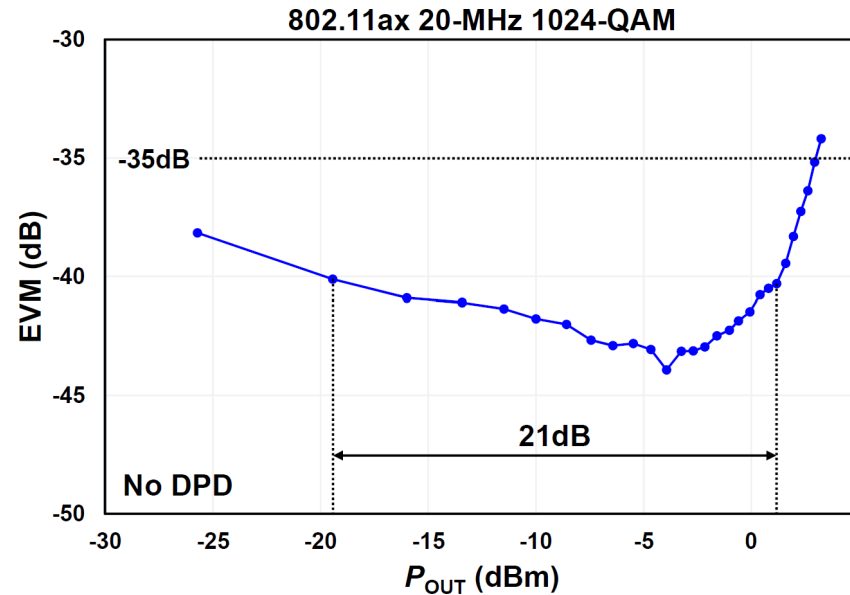


802.11ax 40-MHz 1024-QAM

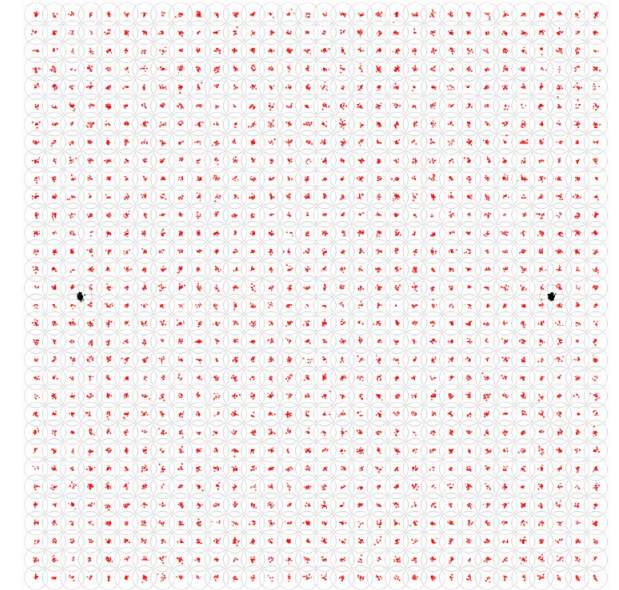



EVM = -42.2dB (@P_{OUT} = -3.0dBm)

- 65nm TX achieves < -40 dB EVM over 21 dB of power backoff
- Full digital transmitter occupies < 0.26mm²

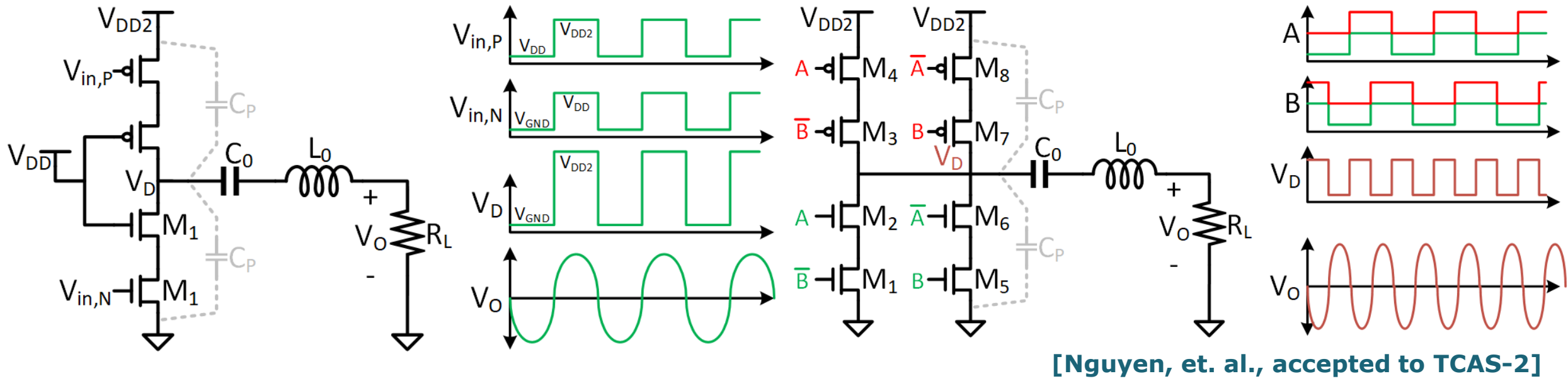- Background and Motivation
- Switched-Capacitor Power Amplifier (SCPA) Introduction
- Recent Demonstrations of SCPAs
- **mmWave SCPAs**
 - **Frequency multiplying class-D**
 - Frequency multiplying SCPA
- Conclusions







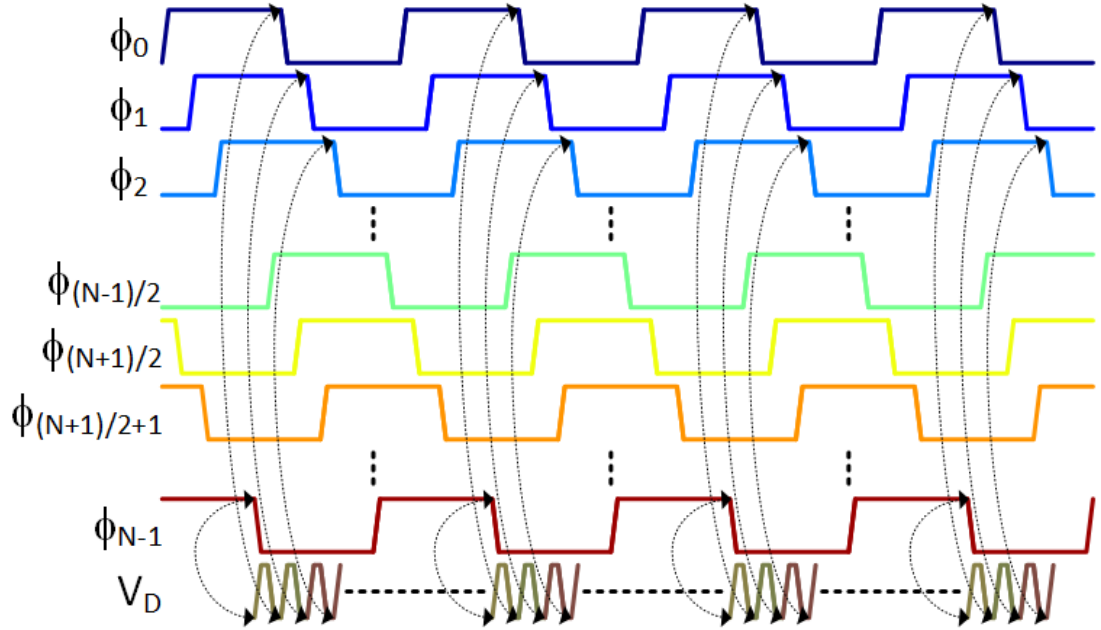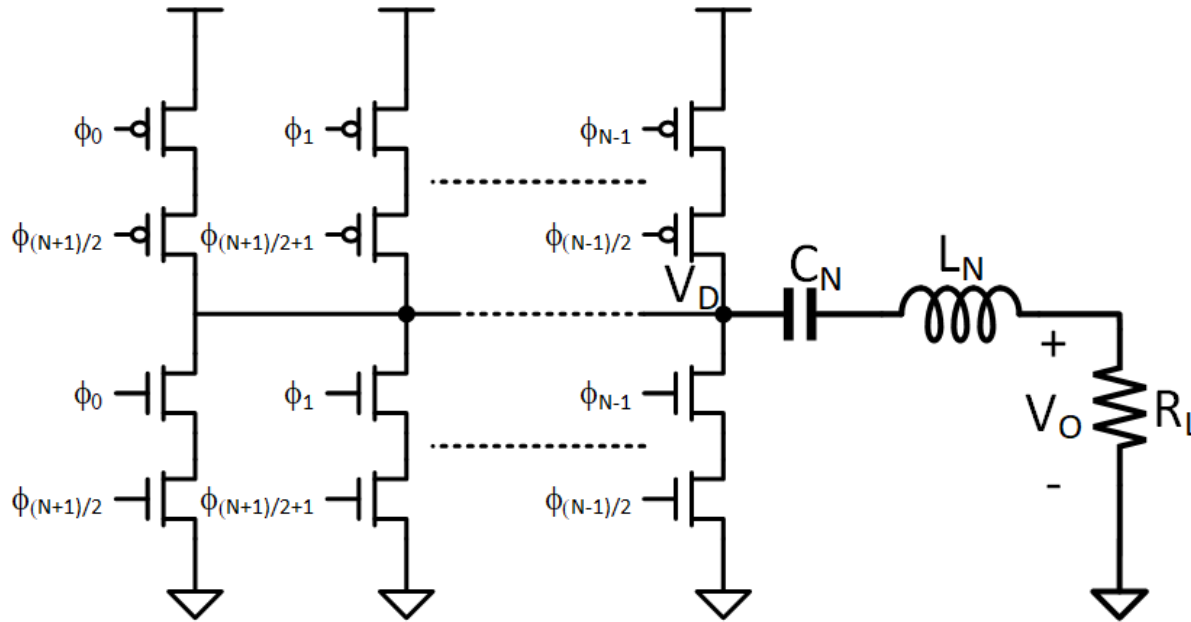- Original SCPA limits high-frequency operation:
 - PMOS transistors are slow
 - Parasitics must be (dis)charged every cycle \rightarrow Power loss $\propto f_{rf}$
- Solution: Use multiple phases in edge-combining (XOR)



[Nguyen, et. al., accepted to TCAS-2]

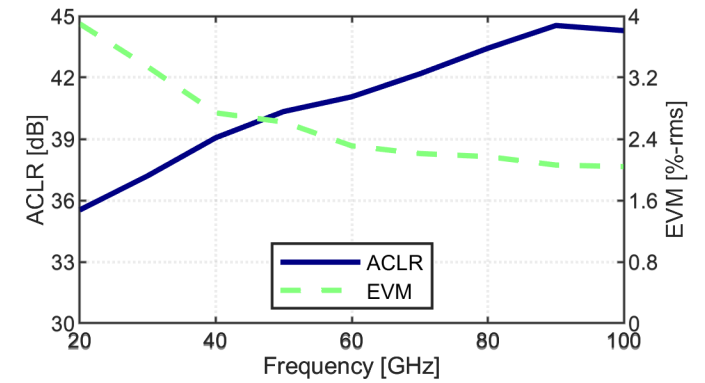  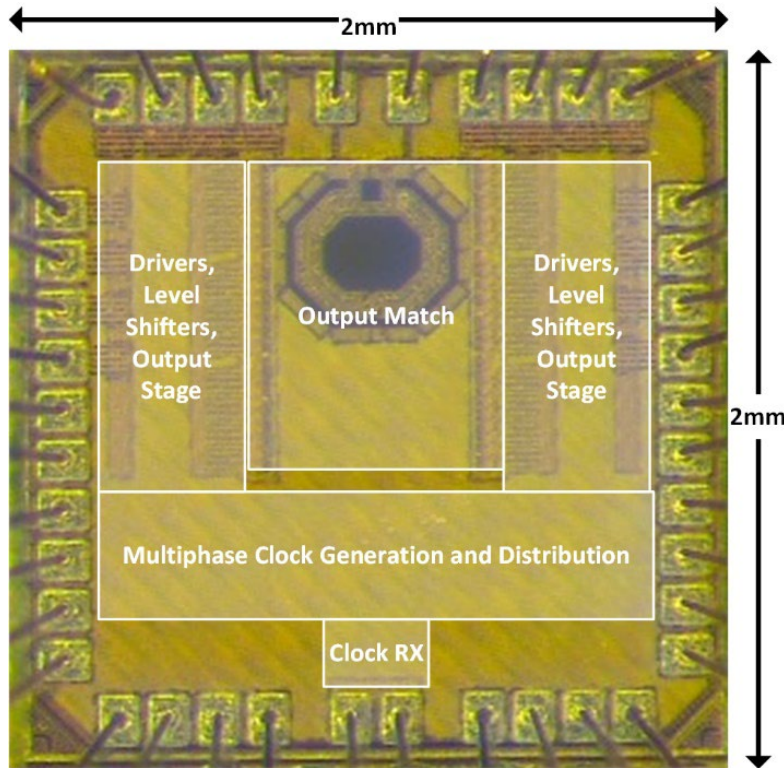- Expand XOR to more than two inputs
- Generalize \rightarrow combining by adding N-branches with N-phases
- Allows reduced frequency clock generation for given output \rightarrow Also, no device must switch at output frequency





Ref.	Topology	Tech.	Supply [V]	Freq. [GHz]	P _{out} [dBm]	SE/PAE/η [%]
This Work	Class-D	65nm	2.4	4.5	22.3	30.2
[17]	Class-D ¹	65nm	2.1	3.3	23	35
[18]	Class-D ¹	65nm	3.0	4.5	26.7	27
[19]	Class-D	180nm	1.8	0.6	21	47

[Nguyen, et. al., accepted to TCAS-2]



- Fabricated 65nm prototype (MiM + UTM)
- Achieves operation at 4.5 GHz (f_{in}=1.5GHz) P_{out} = 22 dBm @ SE = 30%
- Non-CE BPSK modulation shows good EVM/ACLR

 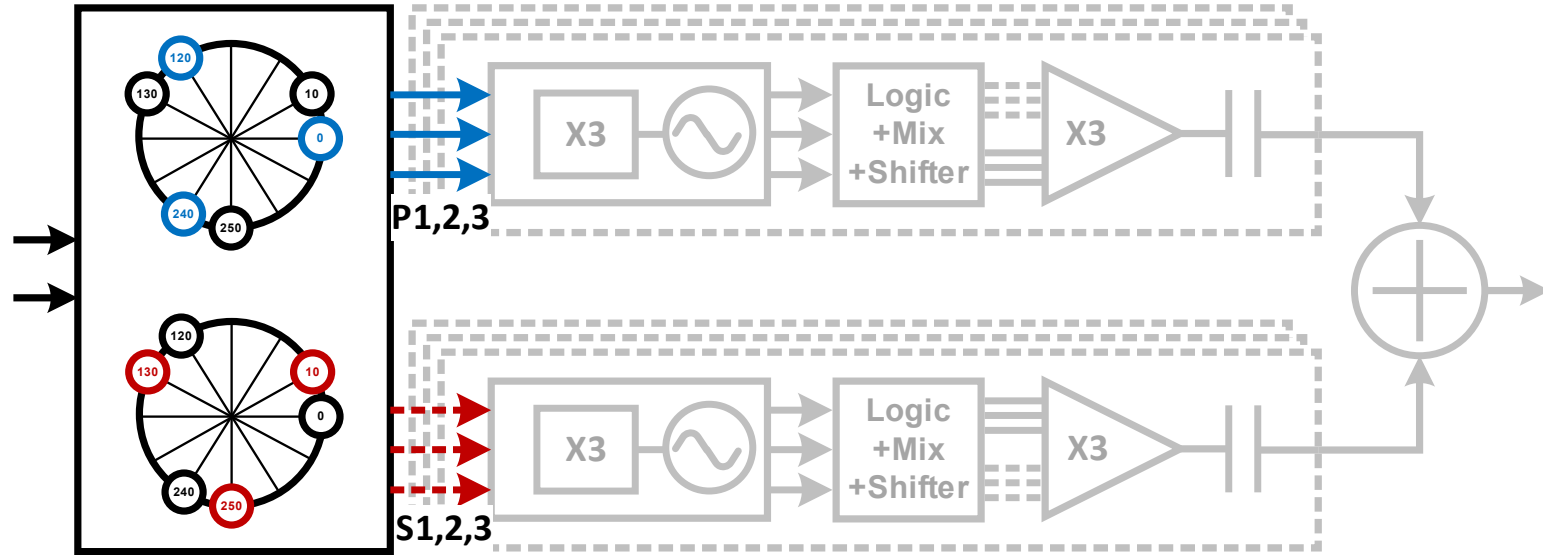- Background and Motivation
- Switched-Capacitor Power Amplifier (SCPA) Introduction
- Recent Demonstrations of SCPAs
- **mmWave SCPAs**
 - Frequency multiplying class-D
 - **Frequency multiplying SCPA**
- Conclusions




[Nguyen, et. al., JSSC 04, 2022]

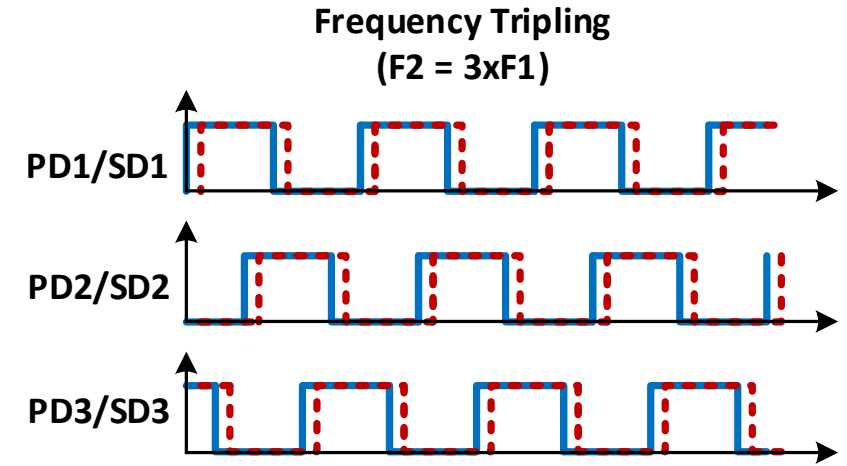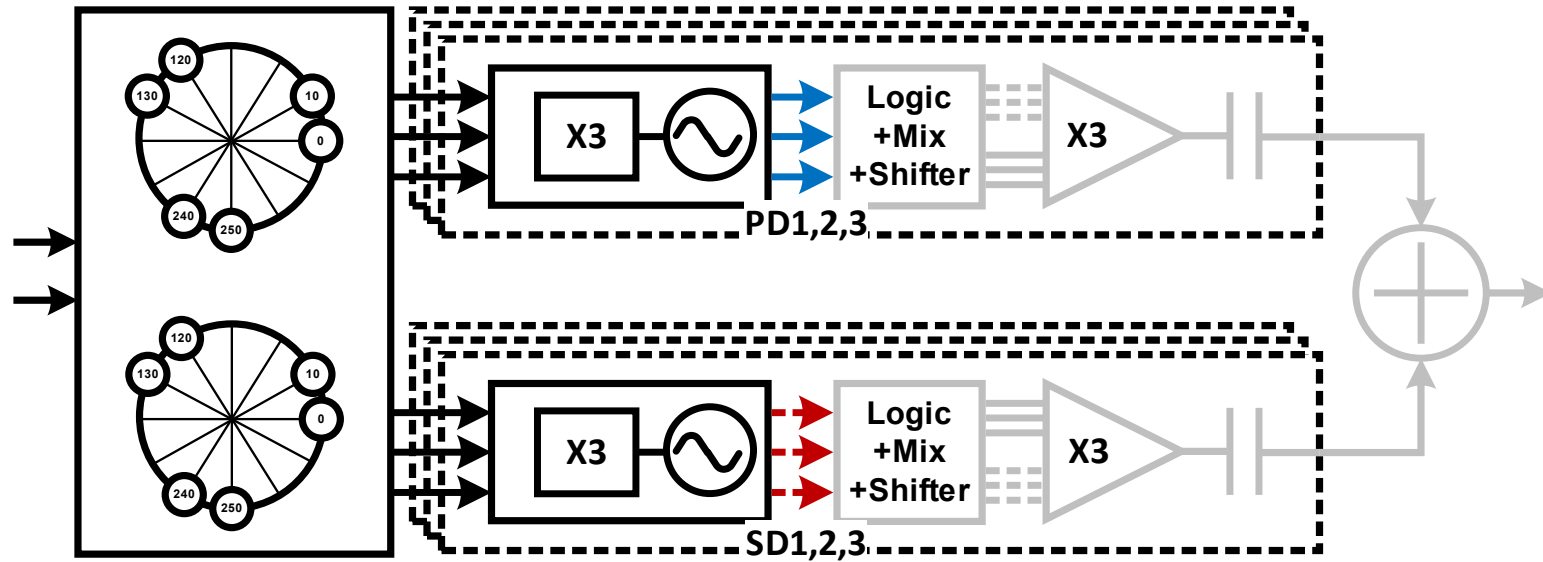
- Twelve phases generated at f_i
- Fed to the Edge-combining DLL network
- Input at $f_i = f_0/9 = 3.111GHz$



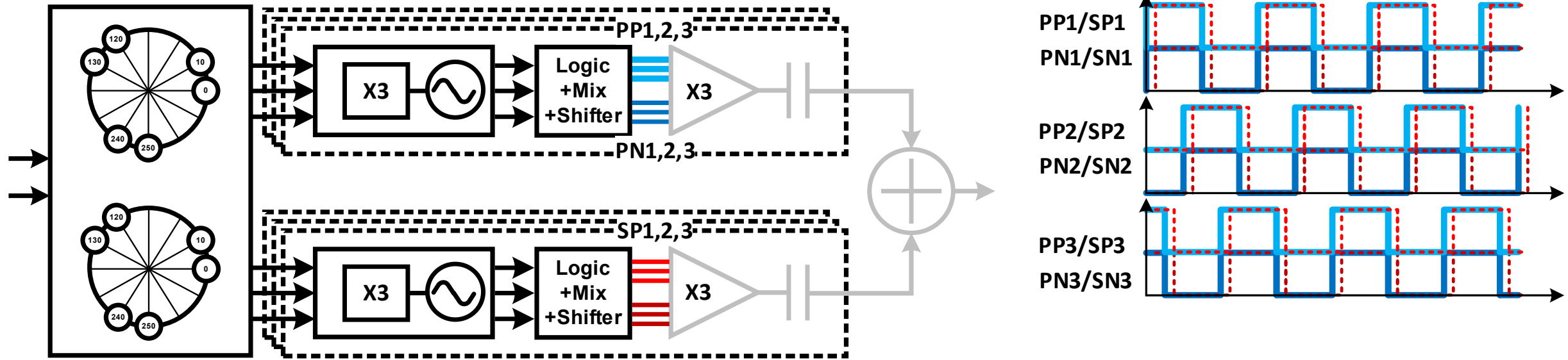
- DLL multiplied frequency by 3
- Multiphased output shifted with 30 degree phase-shifted
- $f_{i2} = f_o/3 = 9.333GHz$
- Tri-phased shifted -> Logic Mixer




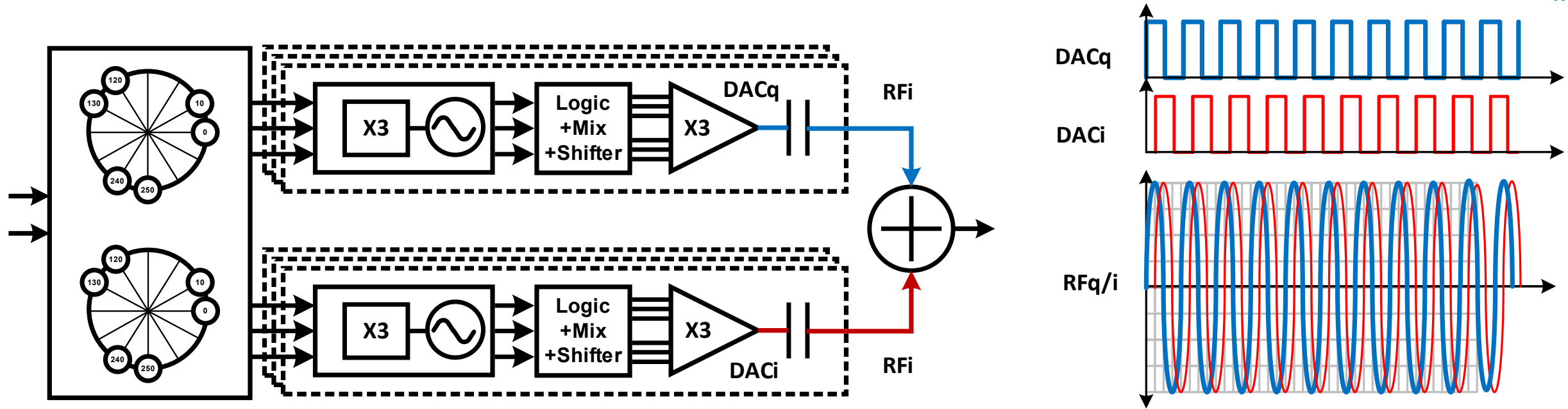- Logic Mixer -> Buffed signal + level shifted signal
- Delay adjusted by the delay chain
- Optimization based exatraction simulation




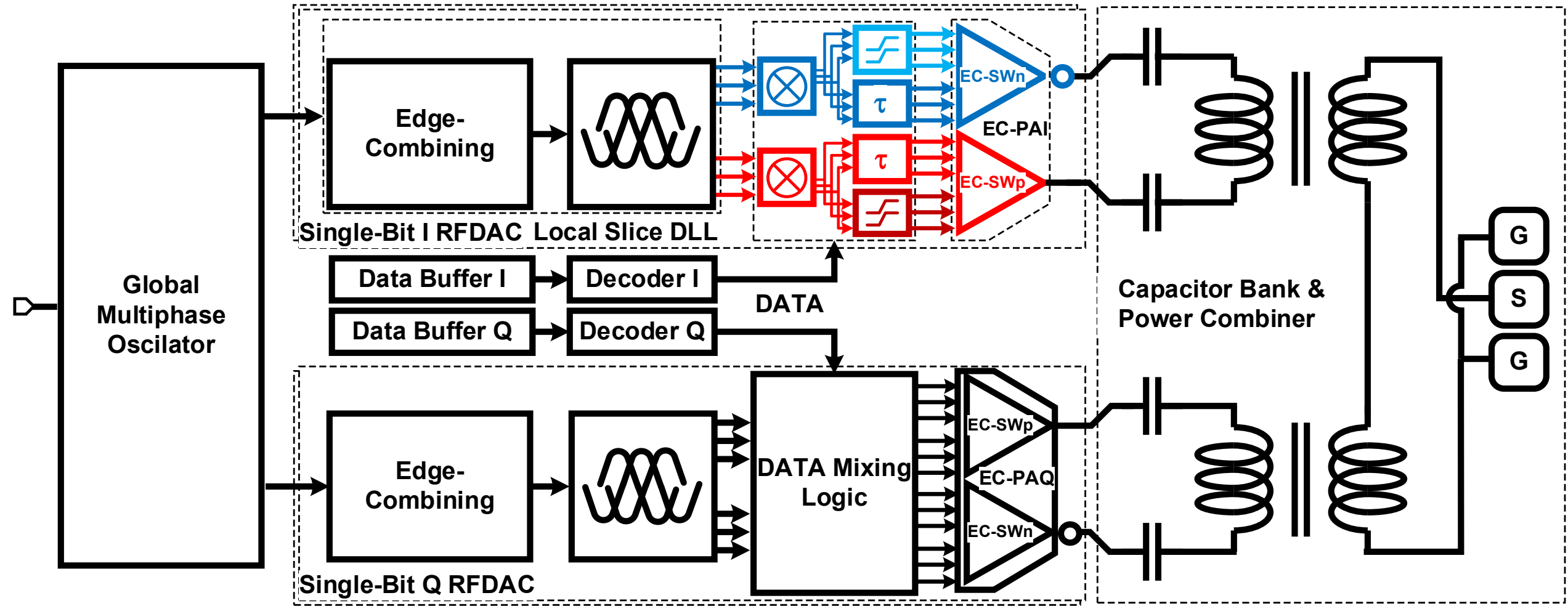- Output phases shifted to 90deg.
- Impedance transformation after the capacitor array
- I/Q combination at the output




 

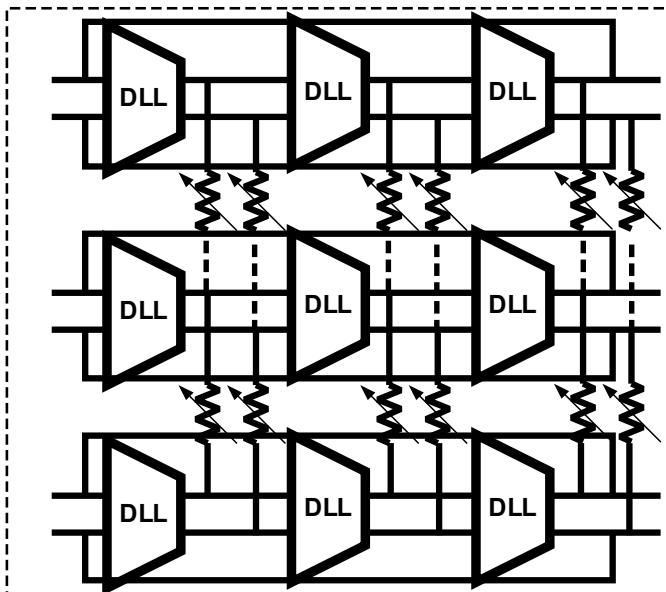
- Euler path for matching unit switched capacitor cell
- Deep-N-Well EGU- SLVT devices are used for faster switching and obtain better performance
- Coupled-DLL network provide in-phases for all unary unit-cells



DLL Matrix Network

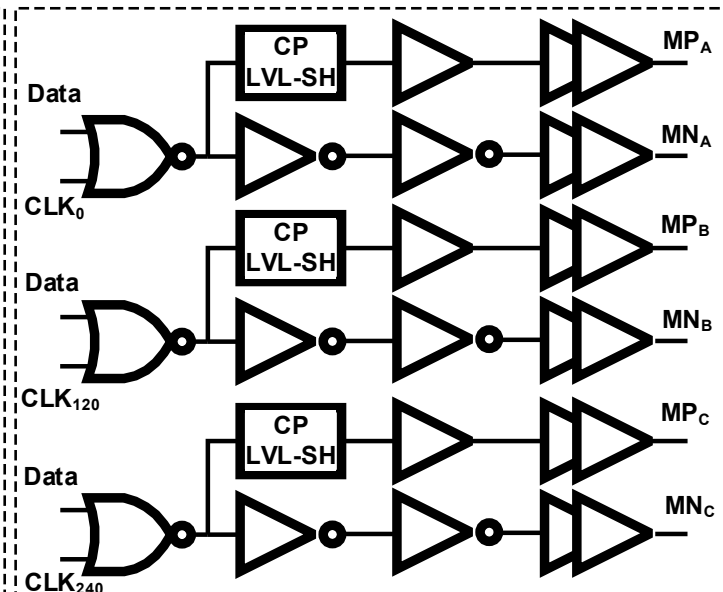




Single-slice-Driver

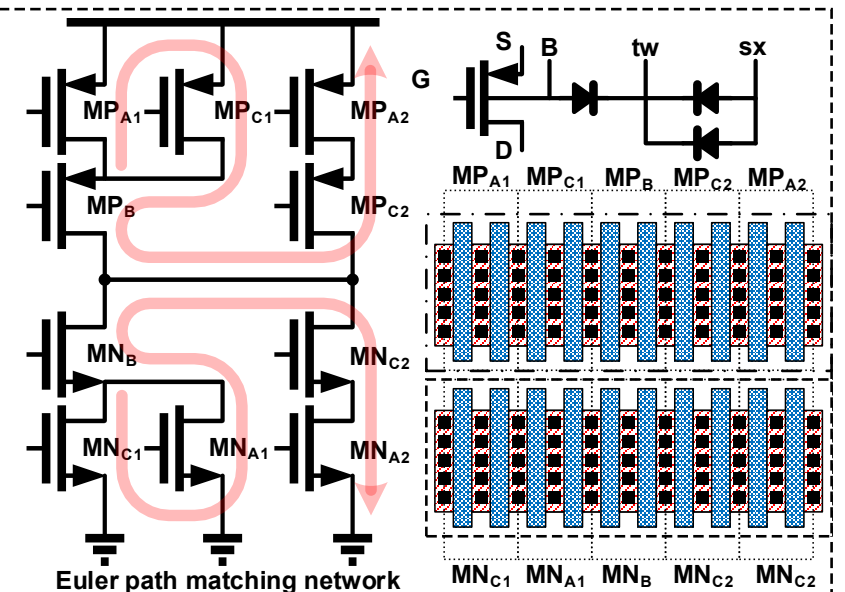

Unit-Cell Construction



mmWave SCPA Layout


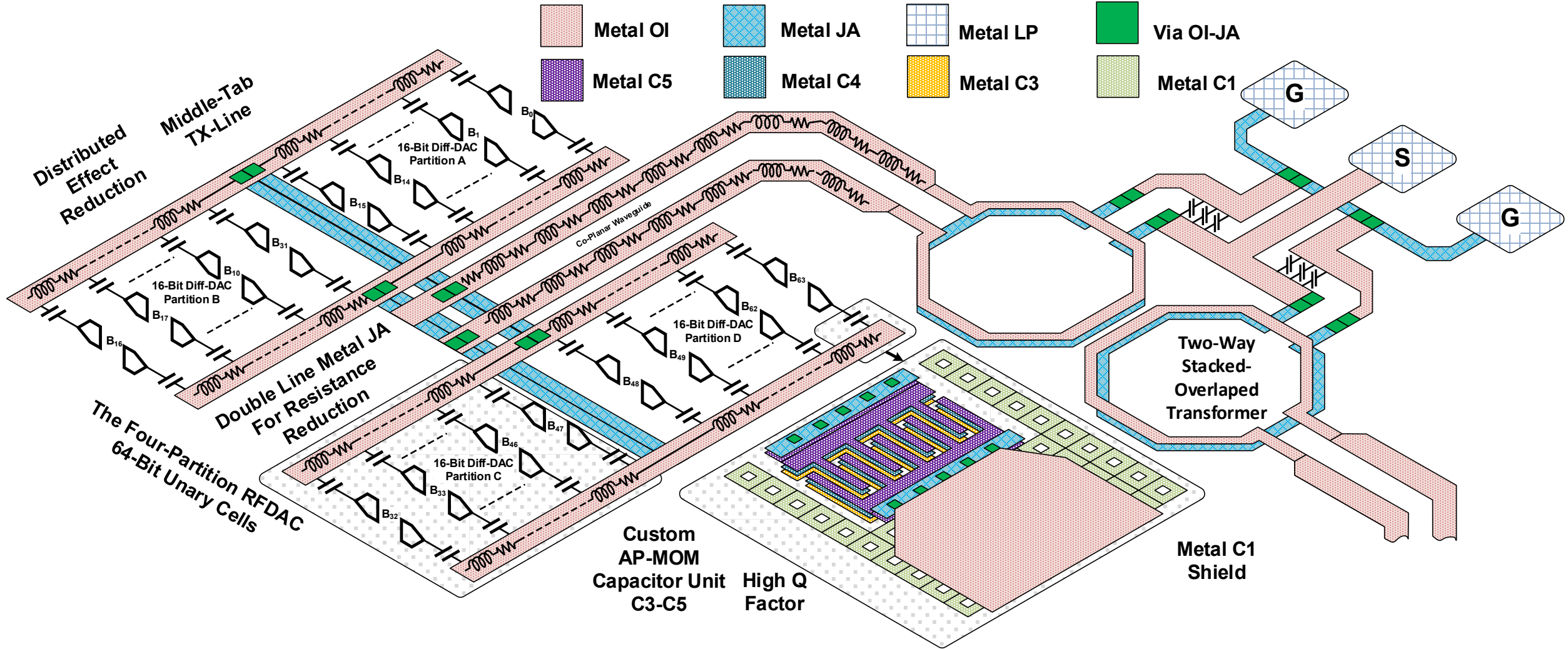


  



- $P_{out} = 21.2\text{dBm @ } 27.9\text{GHz}$
- Drain Efficiency (DE) = 36.7%

- System Efficiency (SE) = 22%

 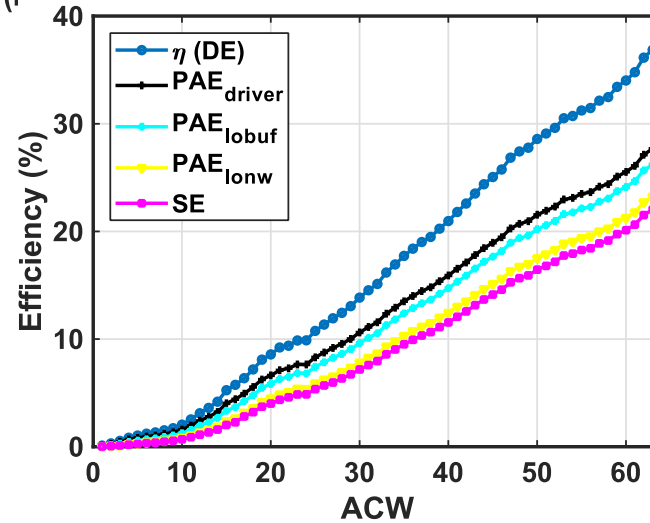

 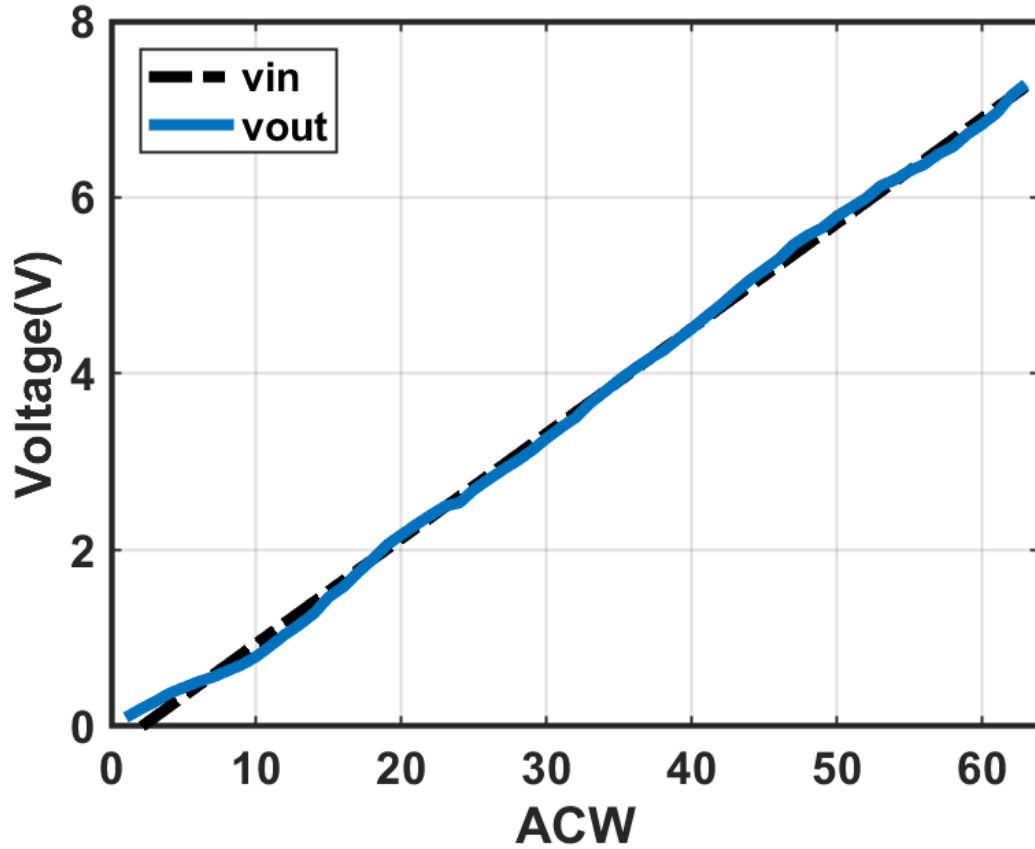

 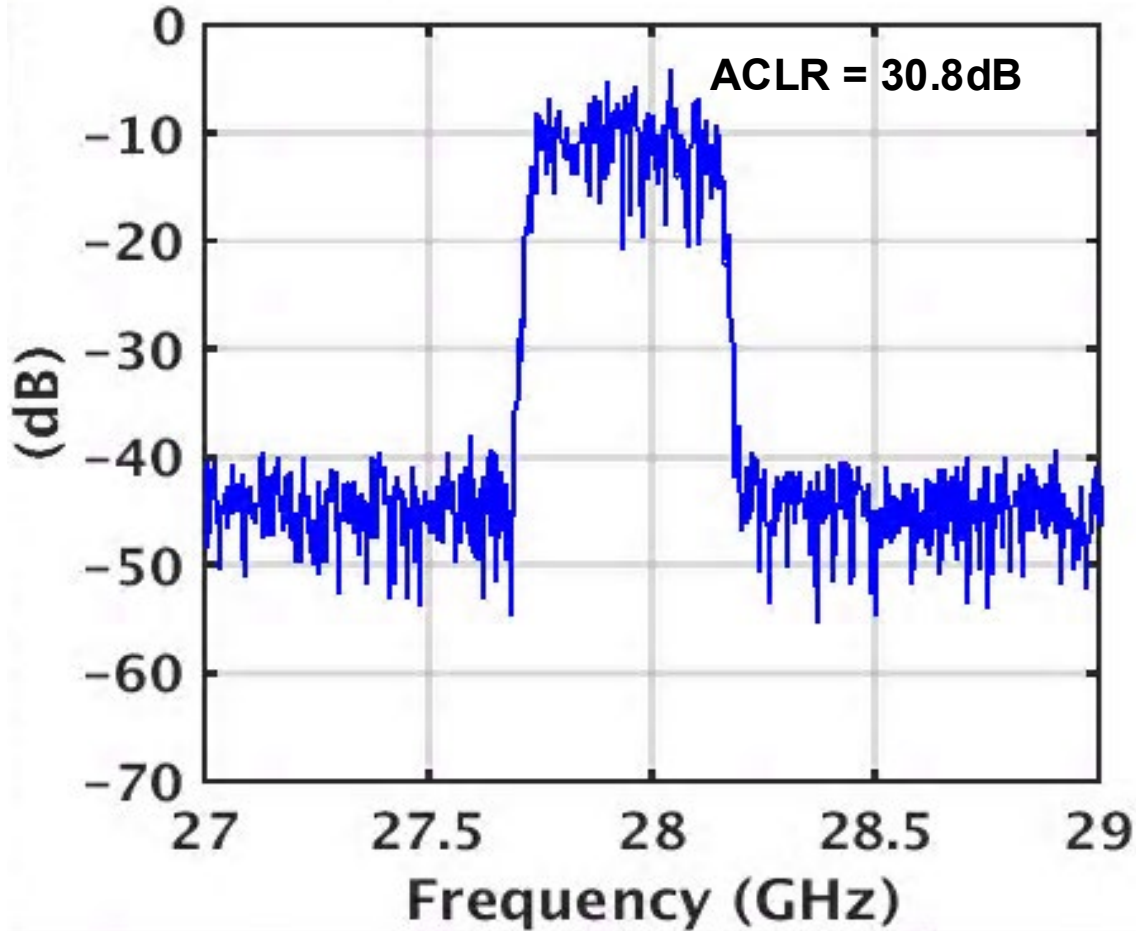- AM – AM obtain nearly perfect linearity
- DNL = +/- 0.5LSB ; INL = +2/-1LSB




- EVM = 3.3% at (2.4Gb/s) with ACLR = 30.8dB

- Background and Motivation
- Switched-Capacitor Power Amplifier (SCPA) Introduction
- Recent Demonstrations of SCPAs
- mmWave SCPAs
 - Frequency multiplying class-D
 - Frequency multiplying SCPA
- **Conclusions**

- SCPAs can be versatile, complete digital transmitters → Baseband to mm-Wave
- SCPAs are inherently linear and do not suffer compression like linear PA and current-mode DPAs
 - Lack of interfaces makes them inherently broadband
 - Switching operation makes them energy efficient
- Frequency limitations can be overcome by embedding frequency multiplication into the output stage



Generic CMOS Power Amplifier

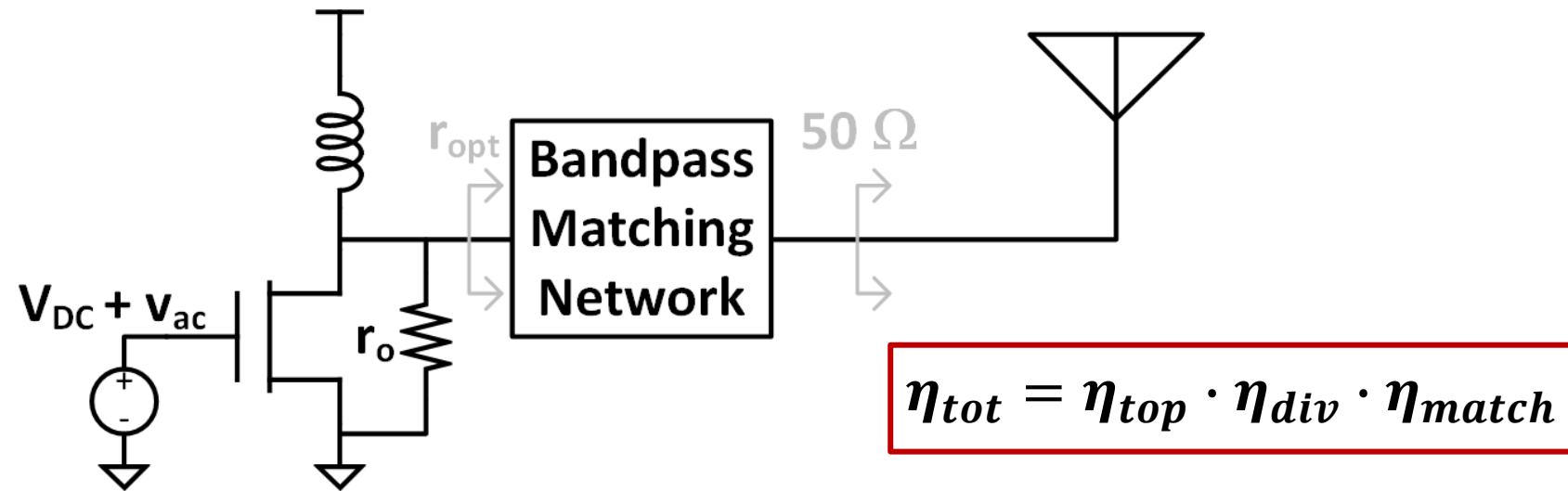

- Three primary drivers of PA efficiency, η :
 - Topology (e.g., class-A, -B, -D, -E, etc.)
 - Voltage/current division at drain node
 - Loss in bandpass impedance matching network

- Topology:
 - Current-mode (A: 50%, B:78.5%)
 - Determined by conduction angle
 - Switching/Voltage Mode (100%)
 - Achieved via pulse shaping
- Matching Network:
 - Losses in passive components (inductors)
 - Q_{NW} \rightarrow dictated by impedance transform:

$$ex.: \eta_{match} = \frac{1 - \frac{Q_{NW}}{Q_{ind,shunt}}}{1 + \frac{Q_{NW}}{Q_{ind,series}}}$$



- Output division:
 - Current division:

$$\eta_{div} = \left(\frac{r_o}{r_{opt} + r_o} \right)^2$$


- Voltage division:

$$\eta_{div} = \left(\frac{r_{opt}}{r_{opt} + r_{sw}} \right)^2$$


 
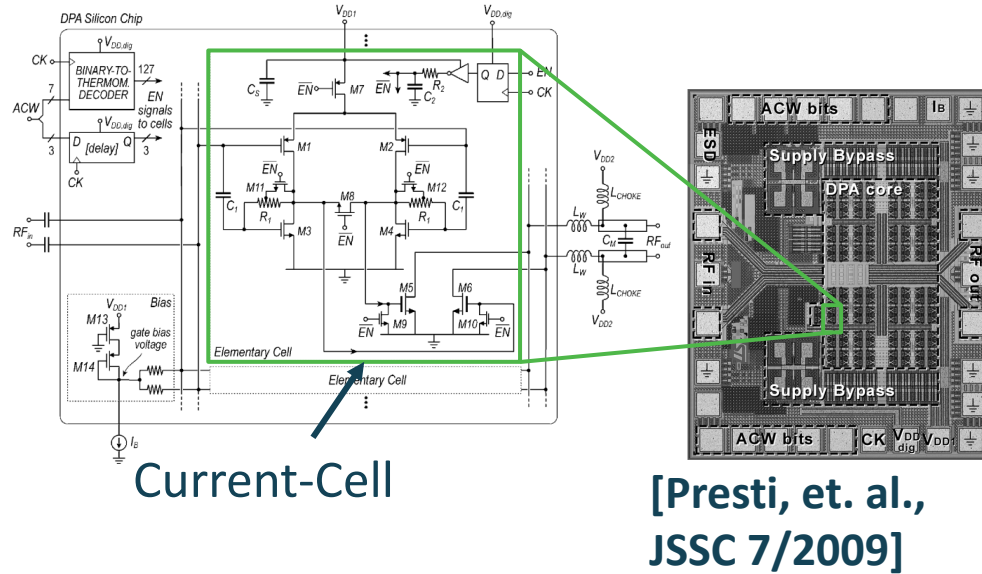
$$Q_{NW} = \sqrt{\frac{R_{antenna}}{R_{opt}} - 1}$$



[Yoo, et. al., JSSC 12/2011]


 


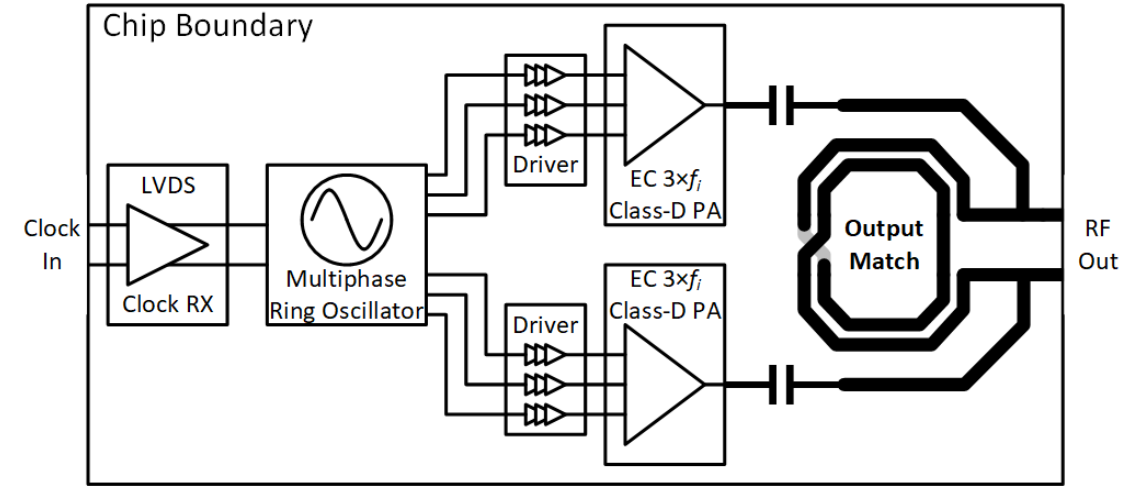  - Single SCPA slice is designed and re-used:
 - Focus on precision timing
 - Optimize one cell and tile it up to desired resolution!
 - No internal analog/RF interfaces!




[Nguyen, et. al., accepted to TCAS-2]

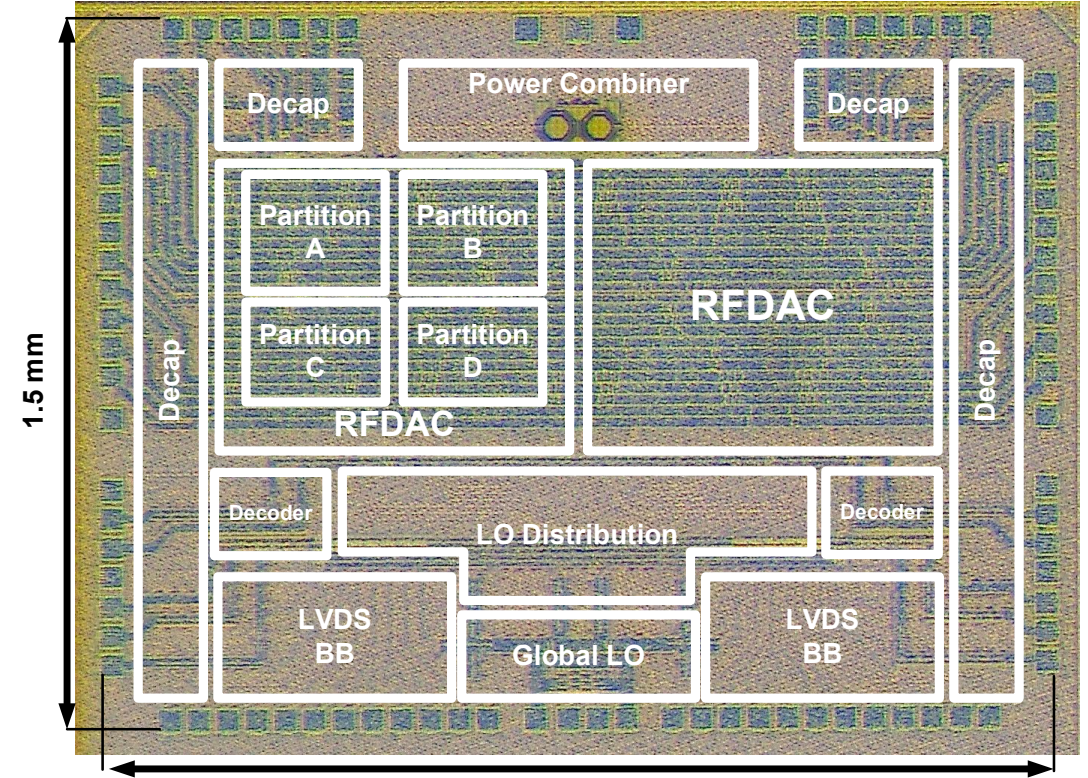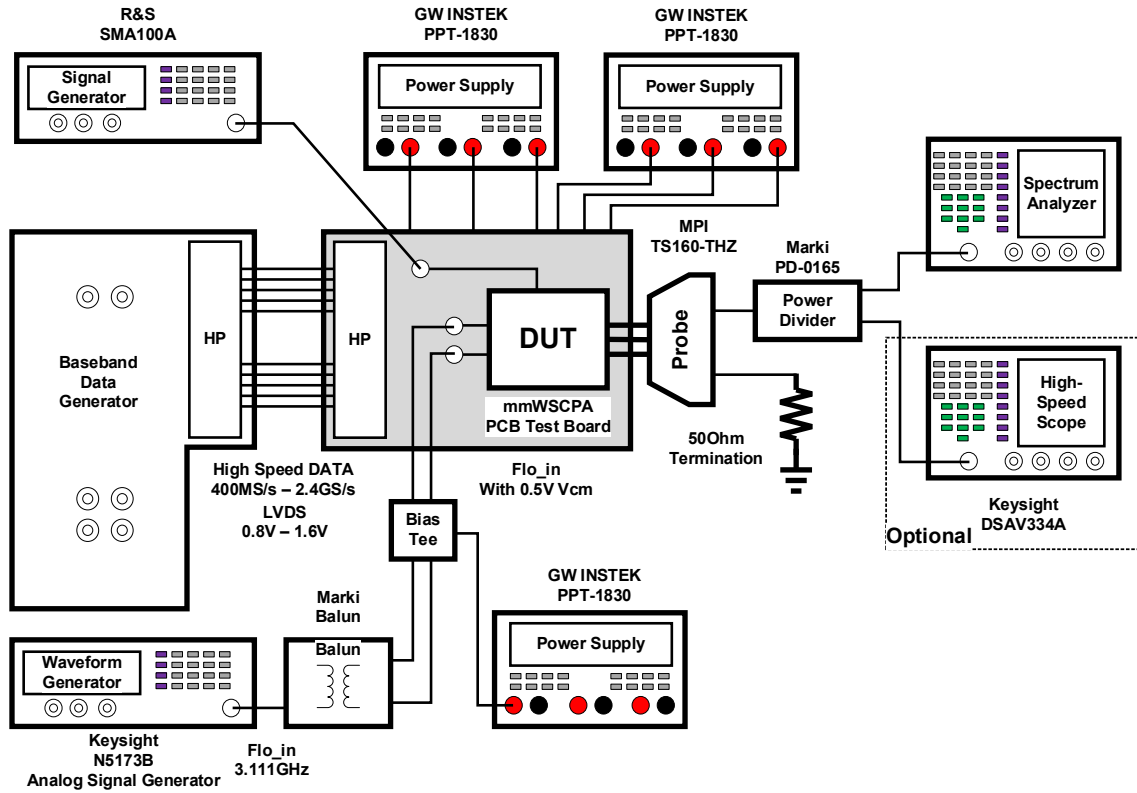- A tripling class-D PA was fabricated to demonstrate potential for Edge-combining
- XOR cell is compacted and reduced to minimize parasitics and save power
- Multiphase signals are generated using multiphase injection locked ring oscillator



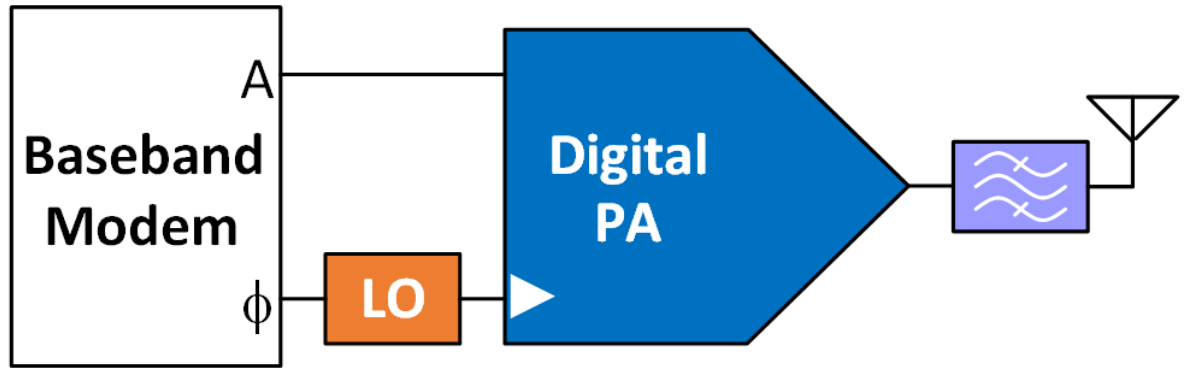- The prototype: 2x1.5mm² on single FDSOI 22nm die
- Output is probed with the T40-THZ MPI
- Chip-on-Board assembly for input signal and power supplies




- In a polar RF DAC, inputs are the amplitude code:

$$A(t) = \sqrt{I^2(t) + Q^2(t)}$$


- The phase modulated RF clock/LO:

$$\phi(t) = \tan^{-1}\left(\frac{Q(t)}{I(t)}\right)$$


- Bandwidth expands due to non-linearity

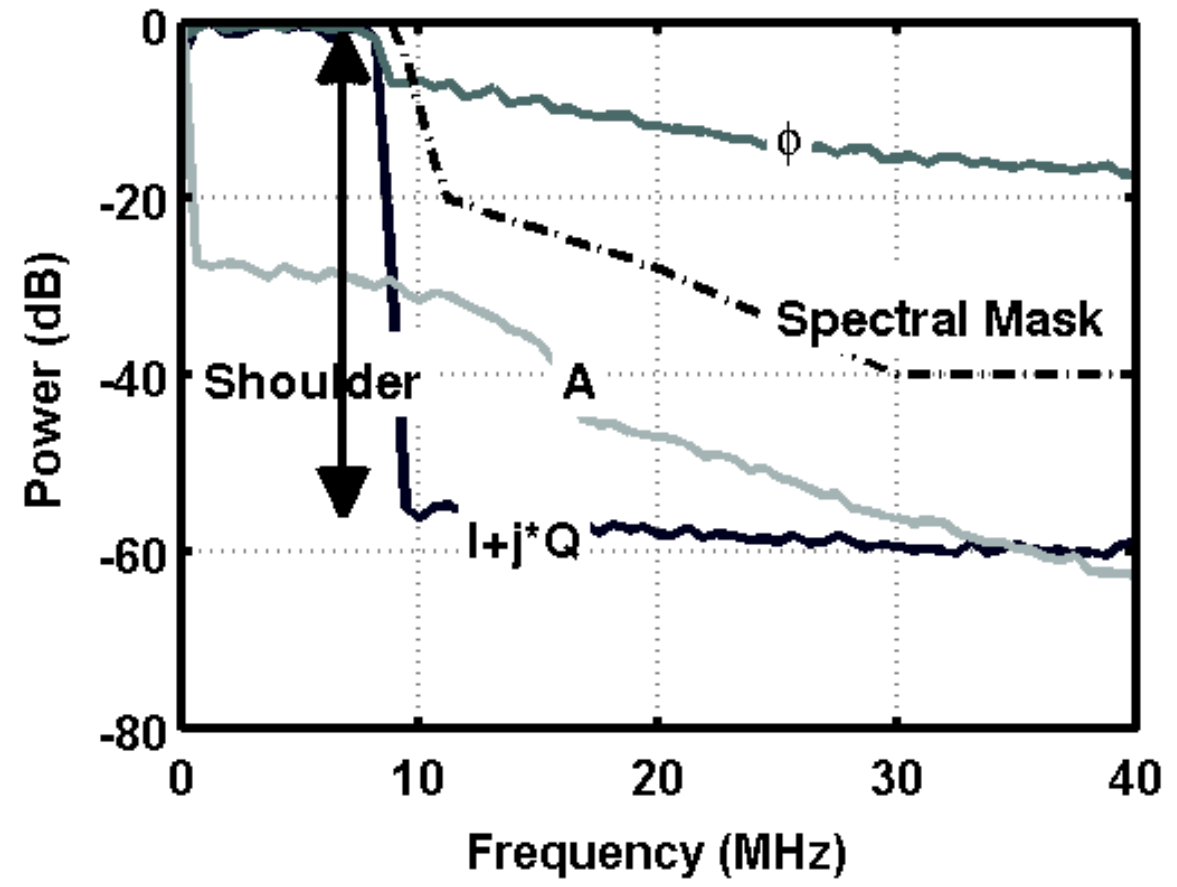

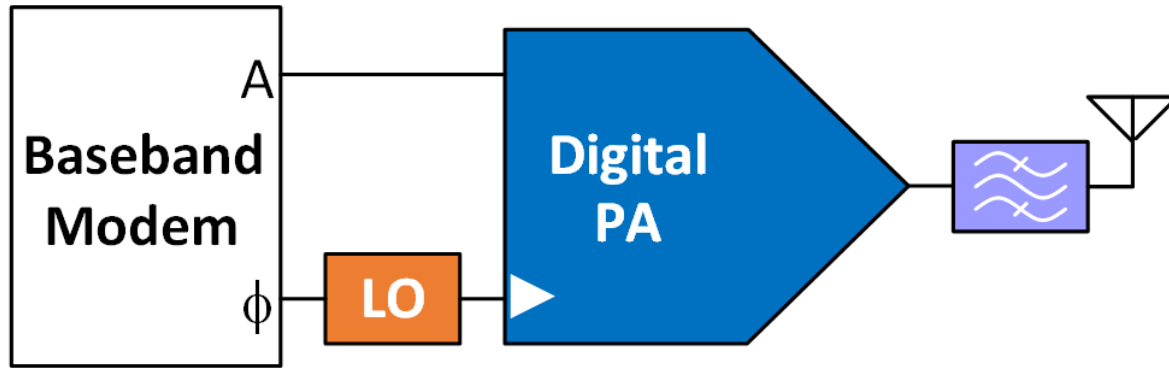How much signal bandwidth do we need to include?




 - Delay between A and ϕ leads to spectral distortion
- Distortion can be estimated as 3rd order intermodulation (IM3D):
- $IM3D \cong 2\pi \cdot (BW_{RF} + \Delta\tau)^2$
 - $BW_{RF} \rightarrow$ Signal Bandwidth
 - $\Delta\tau \rightarrow$ Delay between A and ϕ





[L. Ye, et. al., JSSC 12/2013]

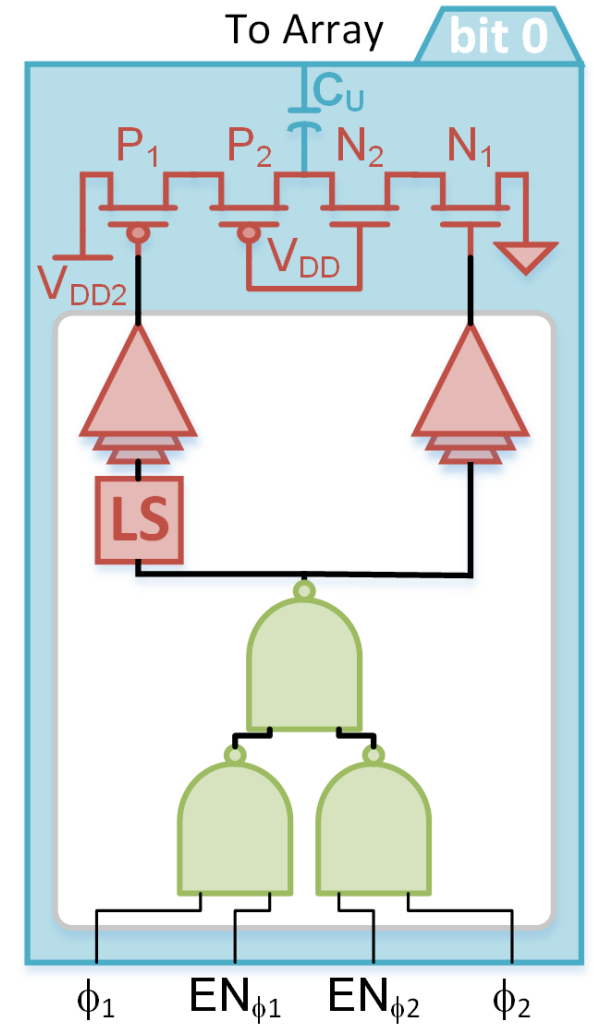- To implement multiphase in an SCPA, only a minor modification to the polar slice:
 - AND gate is replaced by NAND-NAND MUX
 - Logic enforces $EN_{\phi_1} \neq EN_{\phi_2}$
- Synthesized decoder modified to enable switching on phase ϕ_1 or ϕ_2 , or to ground cell
→ fine phase interpolation with amplitude control



 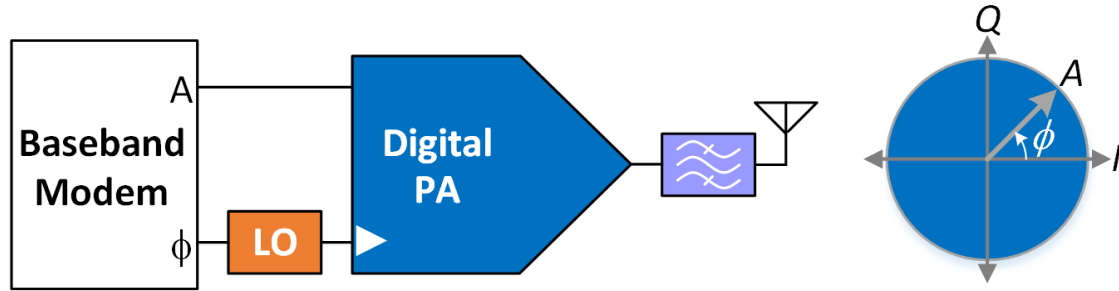[Jin, et. al., ISSCC 2015]
[Yuan, et. al., JSSC 05/2016]



- ✘ Requires conversions from I,Q Baseband to A, ϕ (CORDIC or Look Up Table)
- ✘ Bandwidth Expansion
- ✘ Delay Mismatch
- ✓ Achieves highest power efficiency

- ✓ No baseband conversions are required
- ✓ No bandwidth expansion
- ✓ No delay mismatch
- ✘ -3dB peak output power compared to Polar → reduced efficiency