

List of Illustrations

Fig. 1.1	General structure of active two-stage PFC converter	4
Fig. 1.2	CCM boost PFC front-end and RCD clamped forward output stage	5
Fig. 1.3	General structure of active single-stage PFC converter	6
Fig. 1.4	Integrated DCM single-stage PFC converter with forward output stage	7
Fig. 1.5	DCM S^4 -PFC with bus capacitor voltage V_B feedback	8
Fig. 1.6	CCM integrated single-stage PFC converter (a) CS-CCM (b) VS-CCM	9
Fig. 2.1	Block structure of active PFC converters (a) Two-stage approach. (b) Single-stage approach.	13
Fig. 2.2	General structure of three-terminal single-stage PFC converters	14
Fig. 2.3	Three-terminal integrated single-stage PFC converters (a) DCM S^2 -PFC converter with N_1 feedback (b) CCM current source S^2 -PFC converter (c) CCM voltage source S^2 -PFC converter	15
Fig. 2.4	General structure of 2-terminal single-stage PFC converters	17
Fig. 2.5	Examples of two-terminal single-stage PFC converters	18
Fig. 2.6	Equivalent relationship between three-terminal and two-terminal S^2 -PFC Converters	19
Fig. 2.7	The equivalent relationship between two families of high frequency sources	19
Fig. 2.8	Novel CCM two-terminal single-stage PFC converters	20
Fig. 2.9	The input inductor current waveforms (a) Three-terminal current-source single-stage PFC converter (b) Two-terminal current source single-stage PFC converter	21
Fig. 2.10	The circuit waveforms of conventional diode rectifier	22
Fig. 2.11	The circuit waveforms of DCM single-stage PFC converter with high frequency dither source.	23
Fig. 2.12	Different input inductor currents for DCM and CCM operation	24
Fig. 2.13	Focus on $\langle v_y \rangle$ to study the principle of PFC cell	26
Fig. 2.14	CCM boost PFC converter and its average model	26
Fig. 2.15	Circuit waveforms of the CCM boost PFC average model	28

Fig. 2.16 DCM integrated single-stage PFC waveforms	30
Fig. 2.17 Operate the DCM single-stage PFC converter in CCM mode	31
Fig. 2.19 Circuit waveforms of VS CCM S^2 -PFC converter	32
Fig. 2.20 Input inductor current waveforms	33
(a) Push DCM S^2 -PFC converter into CCM	
(b) VS CCM S^2 -PFC converter	
Fig. 2.21 Circuit waveforms of CS CCM S^2 -PFC converter	34
Fig. 3.1 The current source CCM single-stage PFC converter	37
Fig. 3.2 Operating modes of current source single-stage PFC converter	39
Fig. 3.3 Input current changes from CCM to DCM mode while output power decreases, V_{bus} is limited. (CCM S^2 -PFC converter)	42
Fig. 3.4 Current source single-stage PFC converter with tapping winding	43
Fig. 3.5 L_1 has a strong effect in the CCM input current part	44
Fig. 3.6 Input current waveform (a) 90 Vac low line (b) 230 Vac high line	45
Fig. 3.7 Larger L_1 improves the input power factor in CCM mode (from the point of view of satisfying the PFC condition)	46
Fig. 3.8 L_1 too larger and it will enter CCM mode, hurts PFC	47
Fig. 3.9 Larger L_1 reduce the effective duty cycle D_{eff}	48
Fig. 3.10 L_1 too large will make V_b be lower than V_{in_pk} and hurt the input current waveform.	48
Fig. 3.11 Design optimization approach: fix the total PFC inductance and find the best distribution.	49
Fig. 3.12 Inductance distribution between L_B and L_1 affects the input current THD.	50
Fig. 3.13 Different inductance distribution @ 230 V line, heavy load. ($L_B+L_1 = 1$ mH)	52
Fig. 3.14 Different inductance distribution @ 100 V line, heavy load ($L_B+L_1 = 1$ mH)	52
Fig. 3.15 Different inductance distribution @ 230 V line, heavy load ($L_B+L_1 = 700$ uH)	53
Fig. 3.16 Different inductance distribution @ 230 V line, heavy load ($L_B+L_1 = 1$ mH, 25% tapping winding N_1)	54

Fig. 3.17 Design program block diagram (by Delta INC.)	56
Fig. 3.18 CCM CS S^2 -PFC converter with tapping winding: N1 introduces dead conduction angle and hurts PFC.	59
Fig. 3.19 Comparison of harmonic current of two converters @ $V_{in} = 230\text{ V}$, $P_{in} = 100\text{ W}$, $V_o = 5\text{ V}$	59
Fig. 3.20 Improved CCM S^2 -PFC converter with low-frequency auxiliary switch	60
Fig. 3.21 Control timing of S_r and the improved input inductor current	61
Fig. 3.22 Input inductor current waveforms	64
(a) CCM single-stage PFC converter w/o S_r (25% tapping)	
(b) Improved CCM single-stage PFC converter (25% tapping)	
Fig. 3.23 Harmonic current comparison (a) Low line 100 V (b) high line 230 V	65
Fig. 3.24 Bus capacitor voltage stress comparison	65
Fig. 3.25 The THD and power factor comparison for three different converters	66
Fig. 3.26 Efficiency comparison of three different circuits	66
Fig. 3.27 Harmonic current comparison (different tapping ratio)	67
Fig. 3.28 Efficiencies for different tapping ratio (Improved PFC converter)	68
Fig. 3.29 Implementation variation of the auxiliary switch S_r on the CS single-stage PFC converter	69
Fig. 3.30 Improved CCM CS magnetic switch S^2 -PFC converters with low frequency auxiliary switch.	69
Fig. 3.31 Improved DCM S^2 -PFC converter	70
Fig. 4.1 Active two-stage PFC converter	74
Fig. 4.2 Waveforms of two-stage PFC converter	75
Fig. 4.3 CCM boost PFC front-end and RCD clamped forward output stage	75
Fig. 4.4 Active single-stage PFC converter	76
Fig. 4.5 CCM single-stage PFC converter with ACL forward output stage	78
Fig. 4.6 Waveform of single-stage PFC converter	78
Fig. 4.7 C_B vs. Hold-up time @ $P_o = 100\text{ W}$	81
Fig. 4.8 C_B vs. output power (a) 2-stage PFC (b) single-stage PFC	82
Fig. 4.9 Switch rms current vs. output power	84
Fig. 4.10 PFC diode average current vs. output power	85

Fig. 4.11 Output rectifier diode current vs. output power	86
Fig. 4.12 Input inductor peak current vs. output power	87
Fig. 4.13 Output filter inductance vs. output power	88